

9.16 Voltage Follower (Unity Gain Amplifier)

APJAKTU : 2009-10, 2010-11, 2013-14

- A circuit in which the output voltage follows the input voltage is called **voltage follower circuit**.
- The voltage follower circuit using op-amp is shown in the Fig. 9.16.1.
- The node B is at potential V_{in} .
- The node A is also at the same potential as B i.e. V_{in} according to the concept of virtual ground.

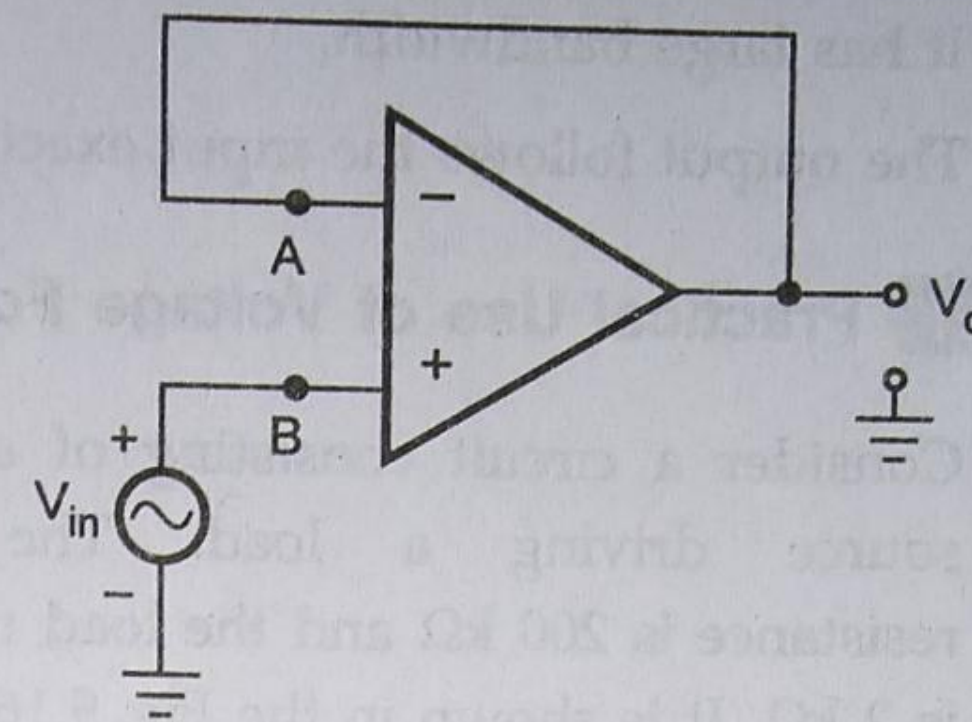


Fig. 9.16.1 Voltage follower

$$\therefore V_A = V_B = V_{in} \quad \dots (9.16.1)$$

- Now node A is directly connected to the output. Hence we can write,

$$V_o = V_A \quad \dots (9.16.2)$$

Equating the equations (9.16.1) and (9.16.2),

$$V_o = V_{in} \quad \dots (9.16.3)$$

- For this circuit, the **voltage gain is unity**.
- Thus the output voltage V_o is equal to the input voltage V_{in} . If V_{in} increases, V_o also increases. If V_{in} decreases, then V_o also decreases. Thus output follows the input hence the circuit is called voltage follower circuit.
- It is also called **source follower, unity gain amplifier, buffer amplifier or isolation amplifier**.
- The input and output waveforms are shown in the Fig. 9.16.2.

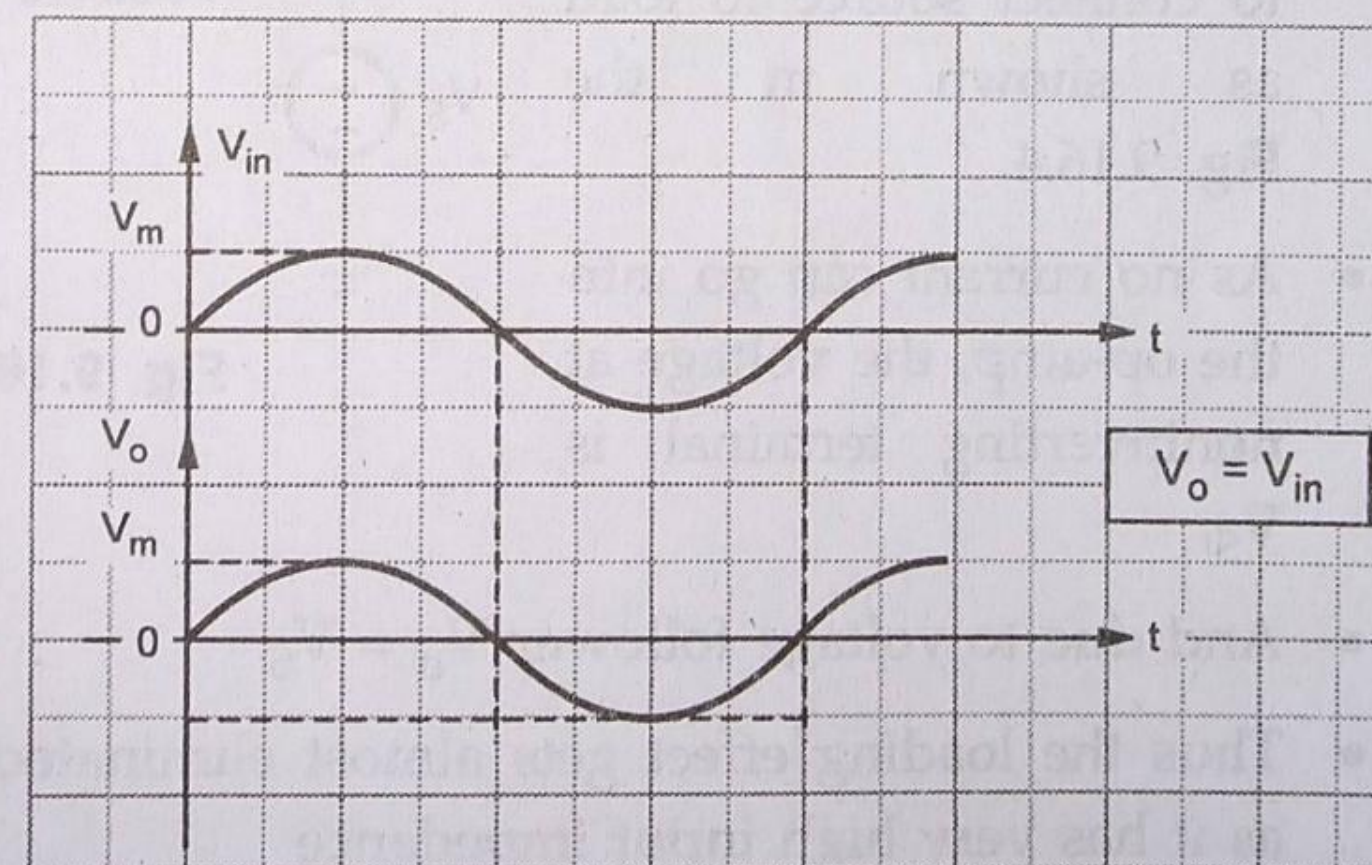


Fig. 9.16.2

Advantages of voltage follower :

- 1) Very large input resistance, of the order of $M\Omega$.
- 2) Low output impedance, almost zero.

- Hence it can be used to connect high impedance source to a low impedance load, as a buffer. This eliminates the loading effect.
- 3) It has large bandwidth.
- 4) The output follows the input exactly without a phase shift.

9.16.1 Practical Use of Voltage Follower

- Consider a circuit consisting of a voltage source driving a load. The source resistance is $200\text{ k}\Omega$ and the load resistance is $2\text{ k}\Omega$. It is shown in the Fig. 9.16.3.
- According to potential divider.

$$V_o = \frac{V_S R_L}{R_S + R_L} = 0.0099 V_S \approx 0.01 V_S$$

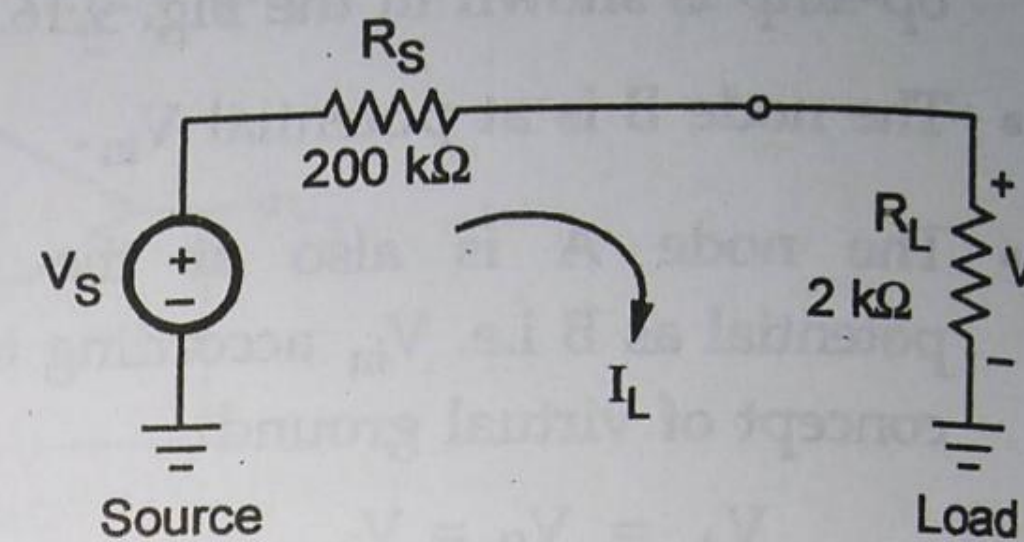


Fig. 9.16.3 Source driving load

- Thus only 0.01 times V_S is available to drive the load and there is severe attenuation. This is nothing but loading effect.
- Now use voltage follower to connect source to load as shown in the Fig. 9.16.4.

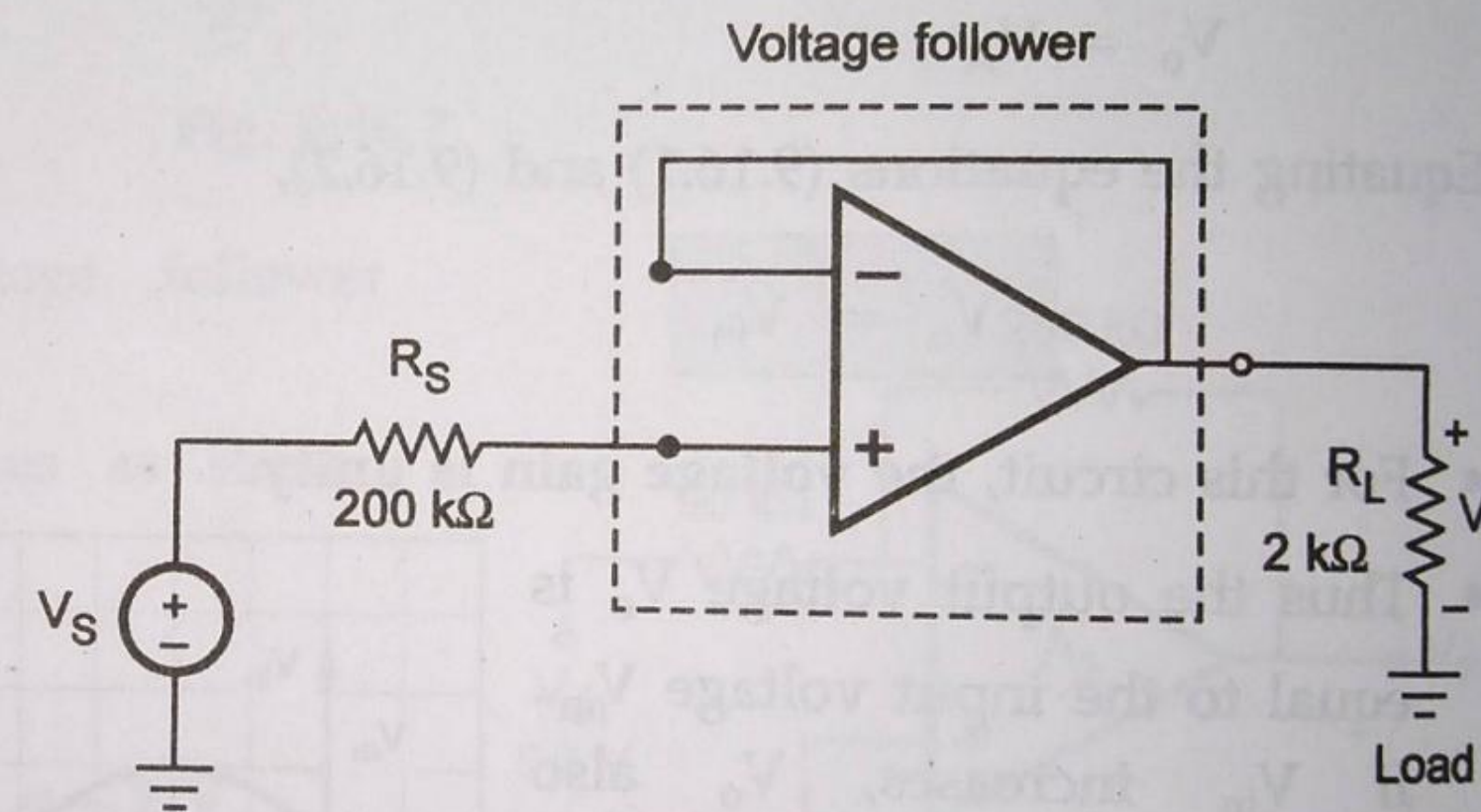


Fig. 9.16.4 Reducing loading effect

- As no current can go into the op-amp, the voltage at noninverting terminal is V_S .
- And due to voltage follower $V_o = V_S$.
- Thus the loading effect gets almost eliminated due to the use of voltage follower as it has very high input impedance.

Review Questions

1. Draw and explain the circuit of unity gain amplifier using op-amp. Where is it used and Why?

APJAKTU : 2009-10, 2010-11, 2013-14, Marks 10

2. State the advantages of voltage follower circuit.