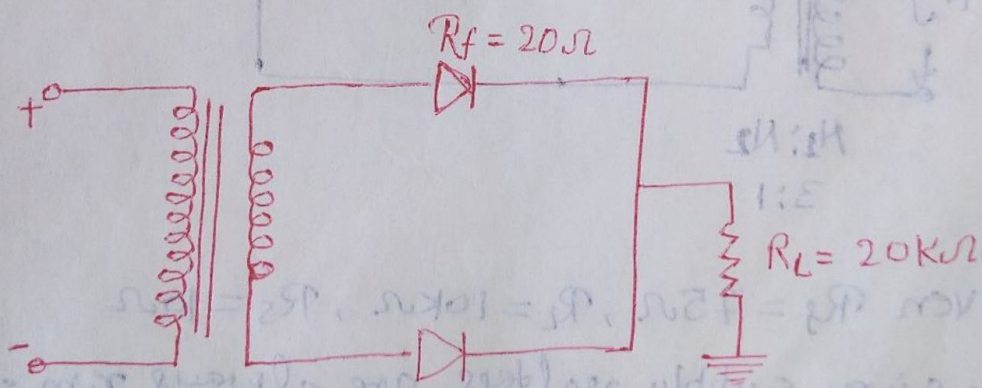


Q. A Centre-tapped is shown below. The voltage across half of the secondary winding is  $V_s = 200 \sin \omega t$ . Find  $I_m$ ,  $I_{dc}$ ,  $I_{rms}$ , ripple factor and PIV.



Sol<sup>n</sup> -  $V_s = 200 \sin \omega t$

$V_m = 200$

$$I_m = \frac{V_m}{R_f + R_L} = \frac{200 \text{ V}}{(0.02 + 20) \text{ k}\Omega} = 9.99 \text{ mA}$$

$$I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 9.99}{\pi} = 6.35 \text{ mA}$$


$$I_{rms} = \frac{I_m}{\sqrt{2}} = 7.06 \text{ mA}$$

$$\text{Ripple factor} = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{(1.11)^2 - 1} = 0.48$$

$$PIV = 2V_m = 2 \times 200 = 400 \text{ V}$$

Q. A half wave rectifier circuit is supplied from a 230V, 50Hz supply with a step down ratio of 3:1 to a resistive load of 10k $\Omega$ . The diode forward resistance is 75 $\Omega$  while transformer secondary resistance is 10 $\Omega$ . Calculate maximum, average, RMS value of current, D.C. output voltage, efficiency of rectification and ripple factor.

Sol<sup>n</sup>

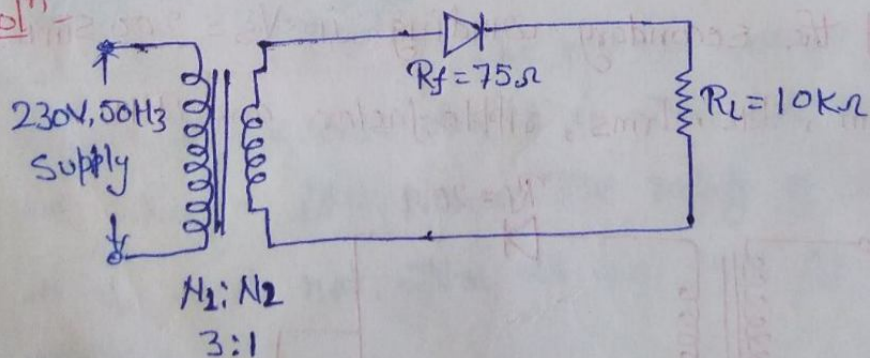

Given  $R_f = 75\Omega$ ,  $R_L = 10\text{k}\Omega$ ,  $R_s = 10\Omega$

The given supply voltage are always r.m.s. value

$$V_p(\text{RMS}) = 230 \text{ V}, \quad \frac{N_2}{N_1} = \frac{1}{3} \Rightarrow V_s = \frac{1}{3} \times 230 = 76.67 \text{ V}$$

$$\therefore \frac{V_s}{V_p} = \frac{N_2}{N_1} \Rightarrow V_s = \frac{1}{3} \times 230 \Rightarrow V_s(\text{RMS}) = 76.67 \text{ V}$$



$$\therefore V_m = \sqrt{2} V_s = \sqrt{2} \times 76.67 = 108.423 \text{ V}$$

$$I_m = \frac{V_m}{R_s + R_f + R_L} = \frac{108.423}{10 + 75 + 10 \times 10^3} = 10.75 \text{ mA}$$

$$I_{dc} \approx I_{av} = \frac{I_m}{\pi} = \frac{10.75}{\pi} = 3.422 \text{ mA}$$

$$I_{rms} = \frac{I_m}{2} = \frac{10.75}{2} = 5.375 \text{ mA}$$

$$\text{dc output voltage, } V_{dc} = I_{dc} R_L = 3.42 \times 10 = 34.22 \text{ V}$$

$$P_{dc} = V_{dc} I_{dc} = 34.22 \times 3.422 \times 10^{-3} = 0.1171 \text{ W}$$

$$\begin{aligned} P_{ac} &= I_{rms}^2 (R_s + R_f + R_L) \\ &= (5.375)^2 [10 + 75 + 10 \times 10^3] \\ &= 0.2913 \text{ W} \end{aligned}$$

$$\% \eta = \frac{P_{dc}}{P_{ac}} \times 100 = \frac{0.1171}{0.2913} \times 100 = 40.19 \%$$

Ripple factor,

$$\begin{aligned} r &= \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{5.375}{3.422}\right)^2 - 1} \\ &= 1.21 \end{aligned}$$