

No. of Printed Pages : 05

Following Paper ID and Roll No. to be filled in your Answer Book.

PAPER ID: 23302Roll
No.

--	--	--	--	--	--	--	--	--	--

B. Tech. Examination 2018-19**(Even Semester)****BASIC ELECTRICAL ENGINEERING*****Time : Three Hours]******[Maximum Marks : 60***

- Note :-**
- (i) This question paper contains three sections.
 - (ii) Section A is compulsory. Section B and C contains internal choices.
 - (iii) Be precise your answer.

SECTION - A

1. Attempt all parts of the following : $8 \times 1 = 8$
- (a) What is basis of Nodal Analysis?
 - (b) What do you mean by bilateral circuit elements?
 - (c) Define form factor.

I.P.T.O.

- (d) What is condition for series resonance?
- (e) Define MMF.
- (f) Which instrument can measure both AC and DC?
- (g) Write number of parallel path in wave winding.
- (h) Single phase induction motor can directly switched on.

SECTION – B

2. Attempt any two parts of the following : $2 \times 6 = 12$

- (a) Determine the value of R_L in Figure-(a) for maximum power transfer and also find maximum power :

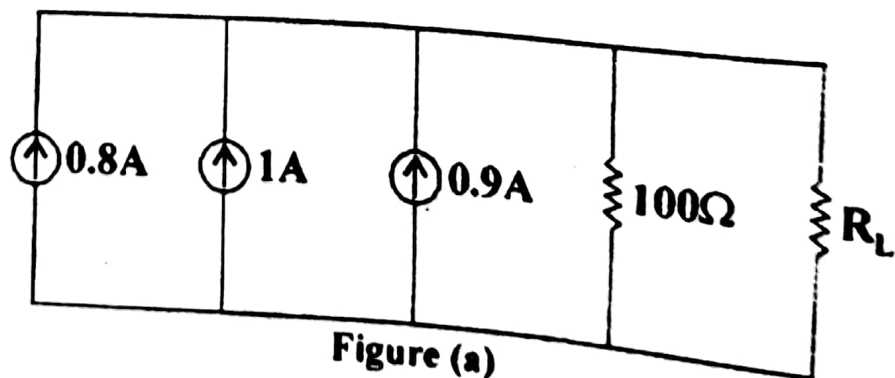


Figure (a)

- (b) Find the average value, rms value and form factor for full wave rectified alternating current.
- (c) Derive the e.m.f. equation of a single phase transformer.

- (d) Derive an expression for torque of a d.c. motor. Also draw torque speed characteristics for d.c. shunt and series motors.

SECTION – C

Note :- Attempt all questions from this section. $10 \times 4 = 40$

3. Attempt any two parts of the following :

- (a) Write the statement of maximum power theorem. Also derive for condition of maximum power. Also find efficiency of circuit on maximum power condition.
- (b) Find out delta to star transformation and vice versa.
- (c) Write the statement of Norton's theorem. Obtain Norton's equivalent circuit at terminal A and B for the network shown in figure-(b) :

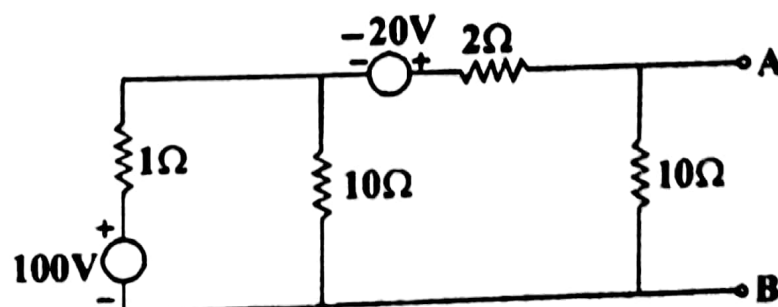


Figure (b)

4. Attempt any two parts of the following :

- (a) Explain the concept of bandwidth and quality factor for series R-L-C circuit. Derive their expressions.
- (b) Find relations between line and phase values for star-delta connection.
- (c) Explain two wattmeter method of measuring three phase power with the help of phasor.

5. Attempt any two parts of the following :

- (a) Describe the construction and working of a single phase induction type energy meter.
- (b) Write similarities and dissimilarities between magnetic and electric circuit.
- (c) A 25 KVA, 2200/200V, single-phase transformer has primary resistance of 1Ω and secondary resistance of 0.01Ω . Find the full load efficiency at 0.8 pf., if the iron loss in the transformer is 200W.

6. Attempt any two parts of the following :
- (a) Derive e.m.f. equation of a d.c. generator. What will be the change in induced e.m.f. if the flux is reduced by 20% and the speed is increased by 20%?
 - (b) Explain the concept of rotating magnetic field also find magnitude and speed of rotating magnetic field. Also explain principle of operation of 3 phase induction motor.
 - (c) Why single phase induction motor is not self starting? Explain any one method of starting.

