
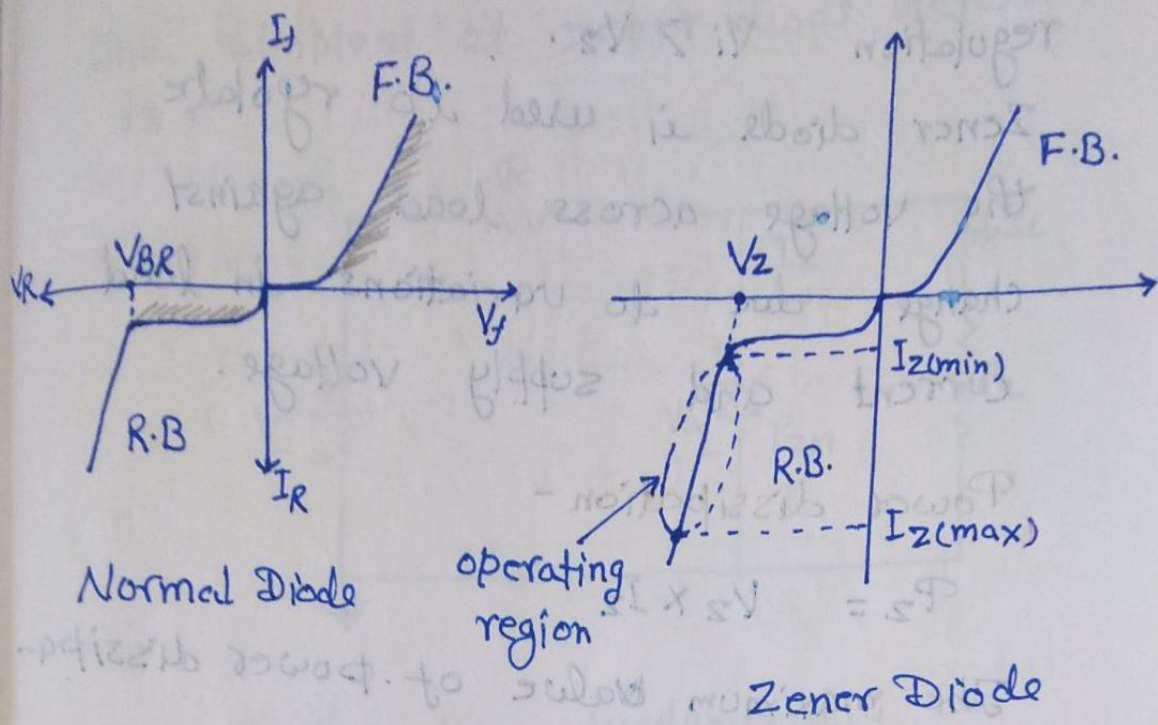


# Zener Diode as a Shunt Regulator →

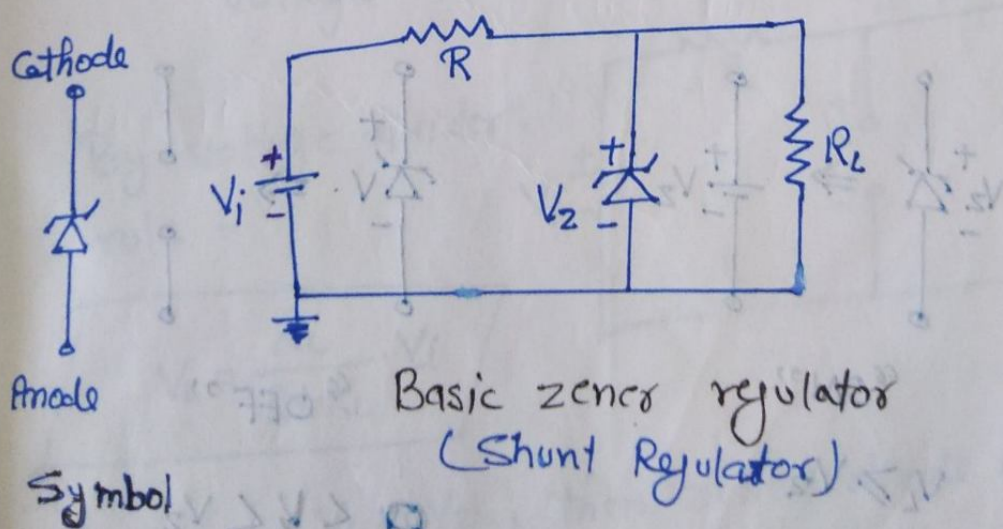

Zener diode works only in reverse biased region and does not work in forward biased. Basic Zener regulator ckt -



For operating the Zener diode as regulation  $V_i > V_z$ .

Zener diode is used to regulate the voltage across load against change due to variations in load current and supply voltage.

Power dissipation -


$$P_z = V_z \times I_z$$

The maximum value of power dissipation is -

$$P_{zm} = V_z \times I_{zm}$$

Where,  $I_{zm}$  = maximum Zener current


Thus

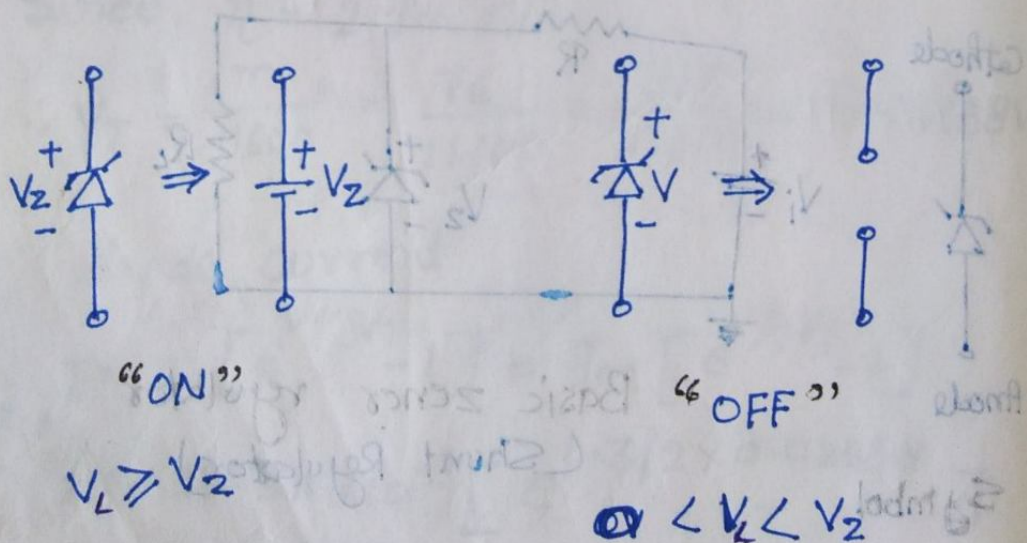



✓ 1.  $V_i$  and  $R_L$  fixed :-

The simplest of zener diode network is -

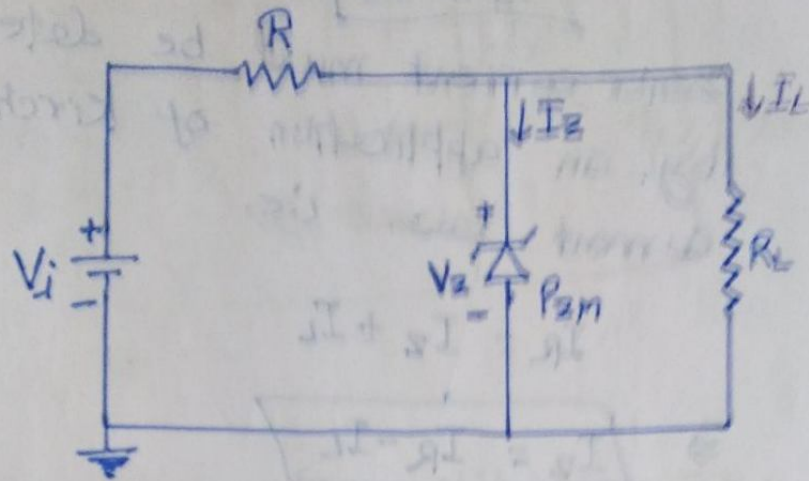


The analysis can fundamentally be broken down into two steps -

Step I - Determine the state of zener by diode removing it from the network and calculating the voltage across the load.

By voltage divider rule -

$$V_L = \frac{R_L}{R + R_L} \cdot V_i$$

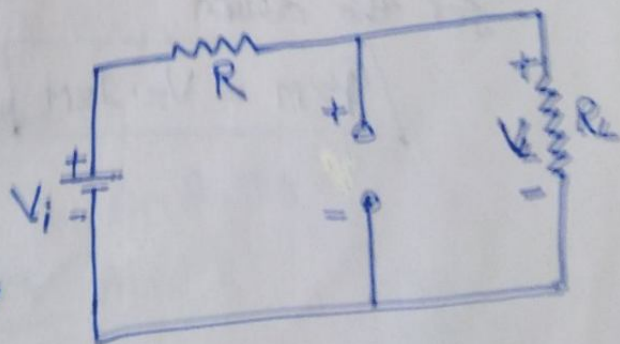

Case 1 - If  $V_L < V_z$ , then zener diode is 'OFF'

Case 2 - If  $V_L \geq V_z$ , then zener diode is 'ON'

Step II - If zener diode is ON then  
we take

$$V_L = V_Z$$

Zener current must be determined  
by an application of Kirchhoff's  
Current law. i.e.

$$I_R = I_Z + I_L$$

$$\Rightarrow I_Z = I_R - I_L$$

Where,

$$I_L = \frac{V_L}{R_L} \text{ and } I_R = \frac{V_R}{R} = \frac{V_i - V_Z}{R}$$

Power dissipated by the zener diode

$$P_Z = V_Z \times I_Z$$

which must be less than the  $P_{ZM}$  specified  
for the device


$$P_{ZM} = V_Z \cdot I_{ZM}$$

$$V = V_L = \frac{R_L}{R + R_L} \cdot V_i$$

Case 1 - If  $V < V_Z$ , then zener diode is OFF.  
Case 2 - If  $V \geq V_Z$ , then zener diode is ON.



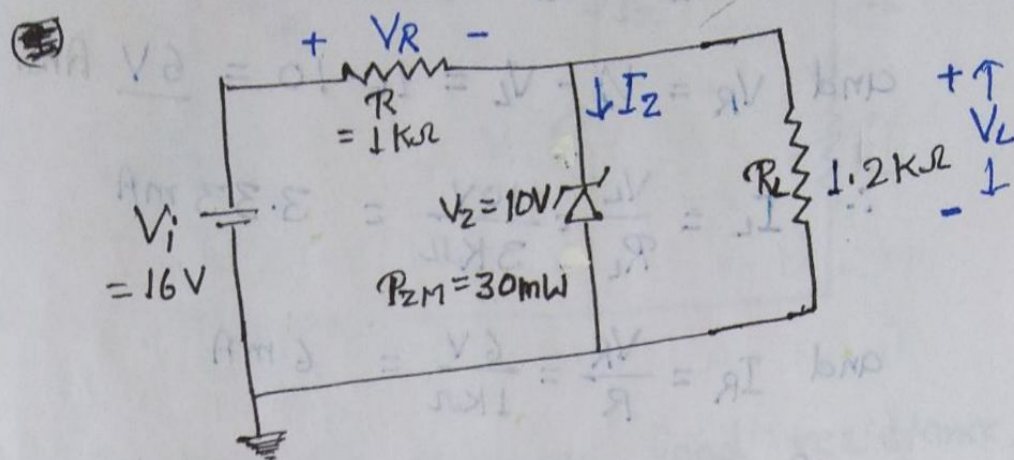✓ Q. For the zener diode network of following fig (a) determine  $V_L$ ,  $V_R$ ,  $I_Z$  and  $P_Z$



(b) Repeat part (a) with  $R_L = 3kΩ$ .

Sol<sup>n</sup> - The voltage across load  $R_L$  i.e.  $V_L$

$$V_L = \frac{R_L}{R + R_L} \cdot V_i = \frac{1.2}{1 + 1.2} \times 16 = 8.73V$$

Since  $V_L (8.73V) < V_z (10V)$ ,  
the zener diode is in "off" state

$$\therefore I_Z = 0A \text{ Ans.}$$

$$V_L = 8.73V \text{ Ans.}$$

$$\therefore V_R = V_i - V_L = 16 - 8.73 \\ = 7.27V \text{ Ans.}$$

$$\text{and } P_Z = V_Z \cdot I_Z = V_Z \times 0 = 0W \text{ Ans.}$$

(b) When  $R_L = 3kΩ$  then

$$V_L = \frac{R_L}{R_L + R} \cdot V_i = \frac{3}{4} \times 16 = 12V$$

Since,  $V_L > V_Z$ , the diode is in "on" state.

$$\therefore V_L = V_Z = \underline{10V} \text{ Ans.}$$

$$\text{and } V_R = V_L - V_Z = 16 - 10 = \underline{6V} \text{ Ans.}$$

$$\therefore I_L = \frac{V_L}{R_L} = \frac{10V}{3K\Omega} = 3.33 \text{ mA}$$

$$\text{and } I_R = \frac{V_R}{R} = \frac{6V}{1K\Omega} = 6 \text{ mA}$$

so that,

$$I_Z = I_R - I_L$$

$$= 6 \text{ mA} - 3.33 \text{ mA}$$

$$= \underline{2.67 \text{ mA}} \text{ Ans.}$$

The power dissipated,

$$P_Z = V_Z \cdot I_Z$$

$$= (10V) \cdot (2.67 \text{ mA})$$


$$= \underline{26.7 \text{ mW}}$$

Which is less than the specified

$$P_{ZM} = 30 \text{ mW}$$



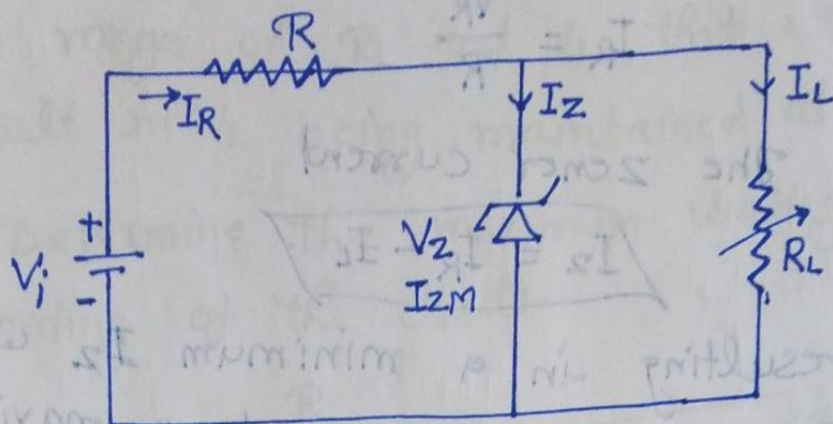2- Fixed  $V_i$  and Variable  $R_L$   $\rightarrow$



To determine the minimum load resistance, ( $R_{L(\min)}$ ) that will turn the Zener diode on, simply calculate the value of  $R_L$  that will result in a load voltage

$$V_L = V_Z \quad \text{c.e.}$$

$$V_L = V_Z = \frac{R_{L(\min)}}{R_{L(\min)} + R} \cdot V_i$$

$$\Rightarrow R_{L(\min)} \cdot V_Z + R V_Z = R_{L(\min)} \cdot V_i$$

$$\Rightarrow R_{L(\min)} [V_i - V_Z] = R V_Z$$

$$\Rightarrow \boxed{R_{L(\min)} = \frac{R \cdot V_Z}{V_i - V_Z}}$$

$$\therefore \boxed{I_{L(\max)} = \frac{V_L}{R_{L(\min)}} = \frac{V_Z}{R_{L(\min)}}$$

Once the diode is in the on state, the voltage across  $R$  remains fixed at

$$V_R = V_i - V_Z$$

and  $I_R$  remains fixed at  $V_Z/R$

$$I_R = \frac{V_Z}{R}$$

The zener current

$$I_Z = I_R - I_L$$

resulting in a minimum  $I_Z$  when  $I_L$  is a maximum and a maximum

$I_Z$  when  $I_L$  is a minimum value

Since  $I_R$  is constant

Since  $I_Z$  is limited to  $I_{ZM}$ ,

$$\therefore I_{L(\min)} = I_R - I_{ZM}$$

and the maximum load resistance is

$$R_{L(\max)} = \frac{V_Z}{I_{L(\min)}}$$

$$R_{L(\min)} = \frac{V_Z}{V_i - V_Z}$$


$$\therefore I_{L(\max)} = \frac{V_Z}{R_{L(\min)}} = \frac{V_Z}{\frac{V_Z}{V_i - V_Z}} = V_i - V_Z$$

Since the diode is in the on state, the voltage across it remains fixed at  $V_Z = V_i - V_L$



Q: For the n/w of following fig., determine the range of  $R_L$  and  $I_L$  that will result in  $V_L$  being maintained at 10V.

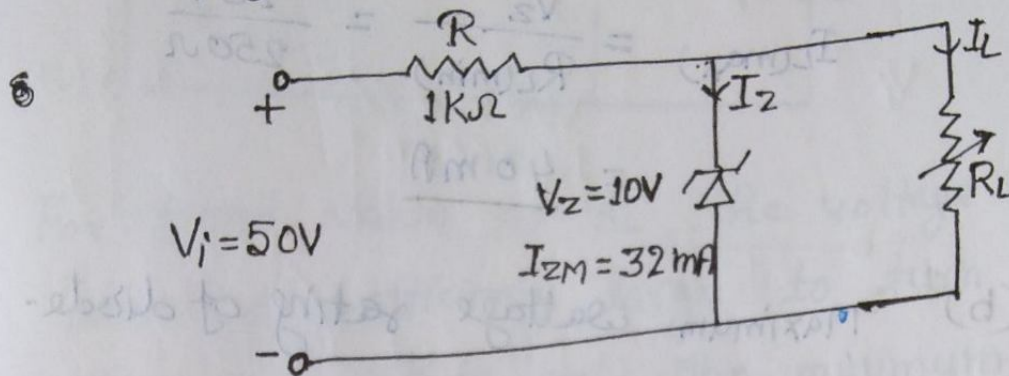(b) Determine the maximum wattage rating of the diode.



Soln- To determine the value of  $R_L$  that will turn on the Zener diode "ON"

$$R_L(\min) = \frac{RV_Z}{V_i - V_Z} = \frac{(1k\Omega)(10V)}{50V - 10V}$$

$$= \frac{10k\Omega}{40} = \underline{250\Omega}$$

The voltage across the resistor  $R$  is the

$$V_R = V_i - V_Z = 50V - 10V = 40V$$

$$\therefore I_R = \frac{V_R}{R} = \frac{40V}{1k\Omega} = 40mA$$

$\therefore$  The minimum level of  $I_L$  is -

$$I_L(\min) = I_R - I_{ZM} = 40 - 32$$

$$= \underline{8mA}$$

Now, the max value of  $R_L$

$$R_{L(max)} = \frac{V_Z}{I_{L(min)}} = \frac{10V}{8mA}$$

$$= \underline{1.25 K\Omega}$$

and max. value of  $I_L$  -

$$I_{L(max)} = \frac{V_Z}{R_{L(min)}} = \frac{10V}{250\Omega}$$

$$= \underline{40mA}$$


(b) Maximum wattage rating of diode-

$$P_{max} = V_Z \cdot I_{ZM}$$


$$= (10V) (32mA)$$

$$= \underline{320mW}$$

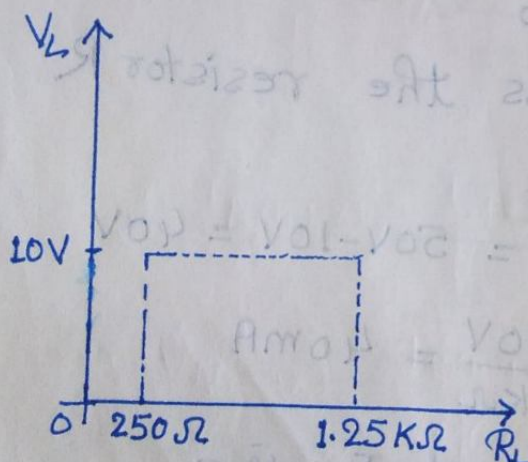A plot of  $V_L$  versus  $R_L$  and  
for  $V_L$  vs  $I_L$  is shown below-




fig(a)

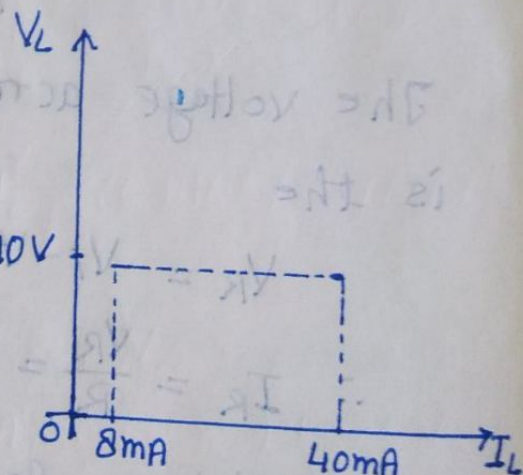

fig(b)


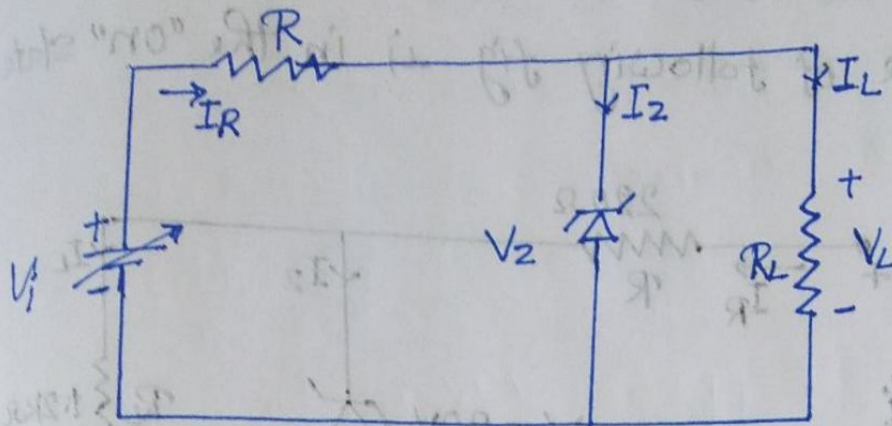
### 3- Variable $V_i$ and fixed $R_L$ $\rightarrow$



For fixed value of  $R_L$ , the voltage  $V_i$  must be sufficiently large to turn the Zener diode on. The minimum turn-on voltage  $V_i = V_{i(\min)}$  is determined

by 
$$V_L = V_Z = \frac{R_L}{R + R_L} \cdot V_i(\min)$$

$$\therefore V_{i(\min)} = \frac{(R + R_L) V_Z}{R_L}$$

Since  $I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \text{fixed}$


Then max. value of  $I_R$  will be :

$$I_{R(\max)} = I_{ZM} + I_L$$

$$\therefore V_{i(\max)} = V_{R(\max)} + V_Z$$

$$\Rightarrow V_{i(\max)} = I_{R(\max)} \cdot R + V_Z$$

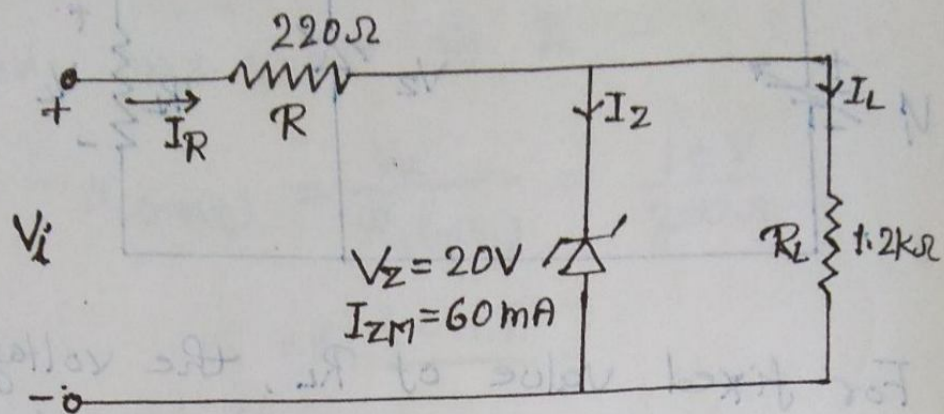Q. Determine the range of values of  $V_i$  that will maintain the Zener diode of following fig in the "on" state



Sol<sup>n</sup> - Minimum value of  $V_i$  is

$$V_L = V_Z = \frac{R_L}{R_L + R} \cdot V_{i(\min)}$$

$$\Rightarrow V_{i(\min)} = \frac{R_L + R}{R_L} \cdot V_Z = \frac{1.2 + 0.220}{1.2} \times 20$$

$$= 23.67V$$

$$\text{Now, } I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{20V}{1.2k\Omega} = 16.67mA$$

$$\therefore I_R(\max) = I_{ZM} + I_L = 60 + 16.67 = 76.67mA$$

$$\begin{aligned} \therefore V_{i(\max)} &= I_R(\max) \cdot R + V_Z \\ &= (76.67mA) \times (0.220k\Omega) + 20V \\ &= 16.87V + 20V \end{aligned}$$

$$= 36.87V$$