

### 9.18 Difference Amplifier or Subtractor

APJAKTU : 2006-07, 2007-08, 2009-10

- The circuit diagram of subtractor is shown in the Fig. 9.18.1.
- To find the relation between the inputs and output let us use Superposition principle.
- Let  $V_{o1}$  be the output, with input  $V_1$  acting alone, assuming  $V_2$  to be zero. And  $V_{o2}$  be the output, with input  $V_2$  acting, assuming  $V_1$  to be zero.
- With  $V_2$  zero, the circuit acts as an inverting amplifier as shown in the Fig. 9.18.2.
- Hence we can write,

$$V_{o1} = -\frac{R_f}{R_1} V_1 \quad \dots (9.18.1)$$

- While with  $V_1$  as zero with  $V_2$  acting, the circuit reduces to as shown in the Fig. 9.18.3.

- This circuit acts as a noninverting amplifier which amplifies the voltage at node B by the factor  $\left(1 + \frac{R_f}{R_1}\right)$ .

- Let potential of node B be  $V_B$ .
- Applying voltage divider rule to the input  $V_2$  loop,

$$V_B = \frac{R_f}{R_2 + R_f} V_2 \quad \dots (9.18.2)$$

$$\therefore V_{o2} = \left[1 + \frac{R_f}{R_1}\right] V_B \quad \dots (9.18.3)$$


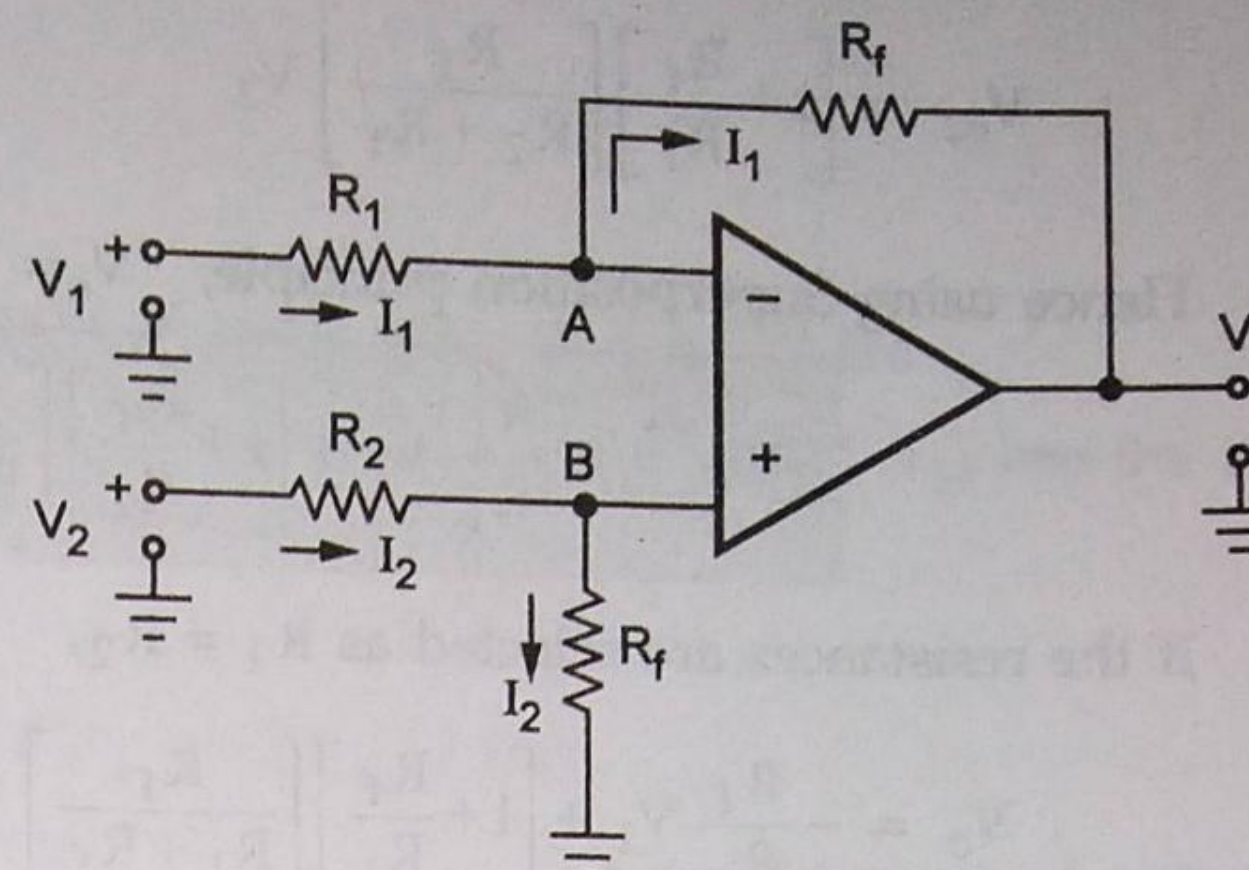
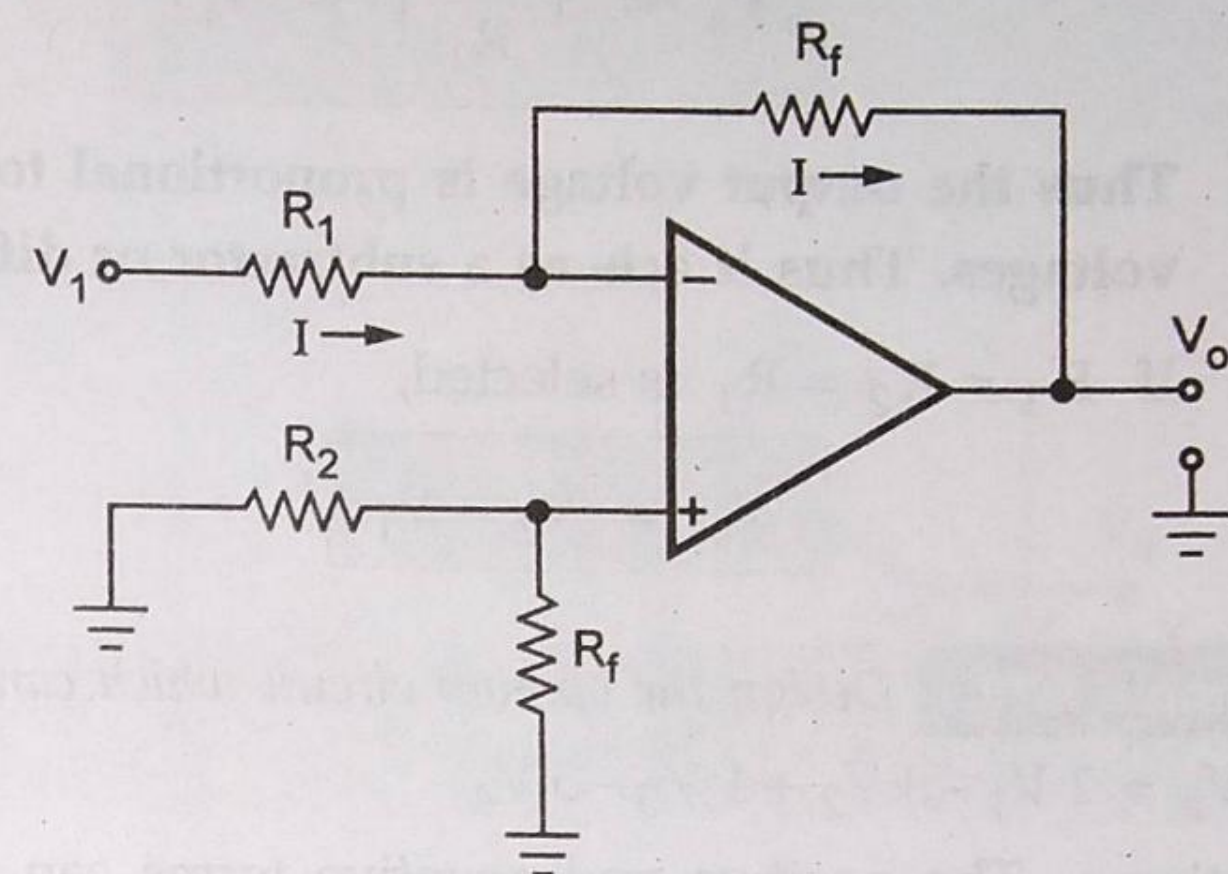


Fig. 9.18.1 Subtractor circuit

Fig. 9.18.2  $V_1$  acting,  $V_2 = 0$ Fig. 9.18.3  $V_2$  acting,  $V_1 = 0$

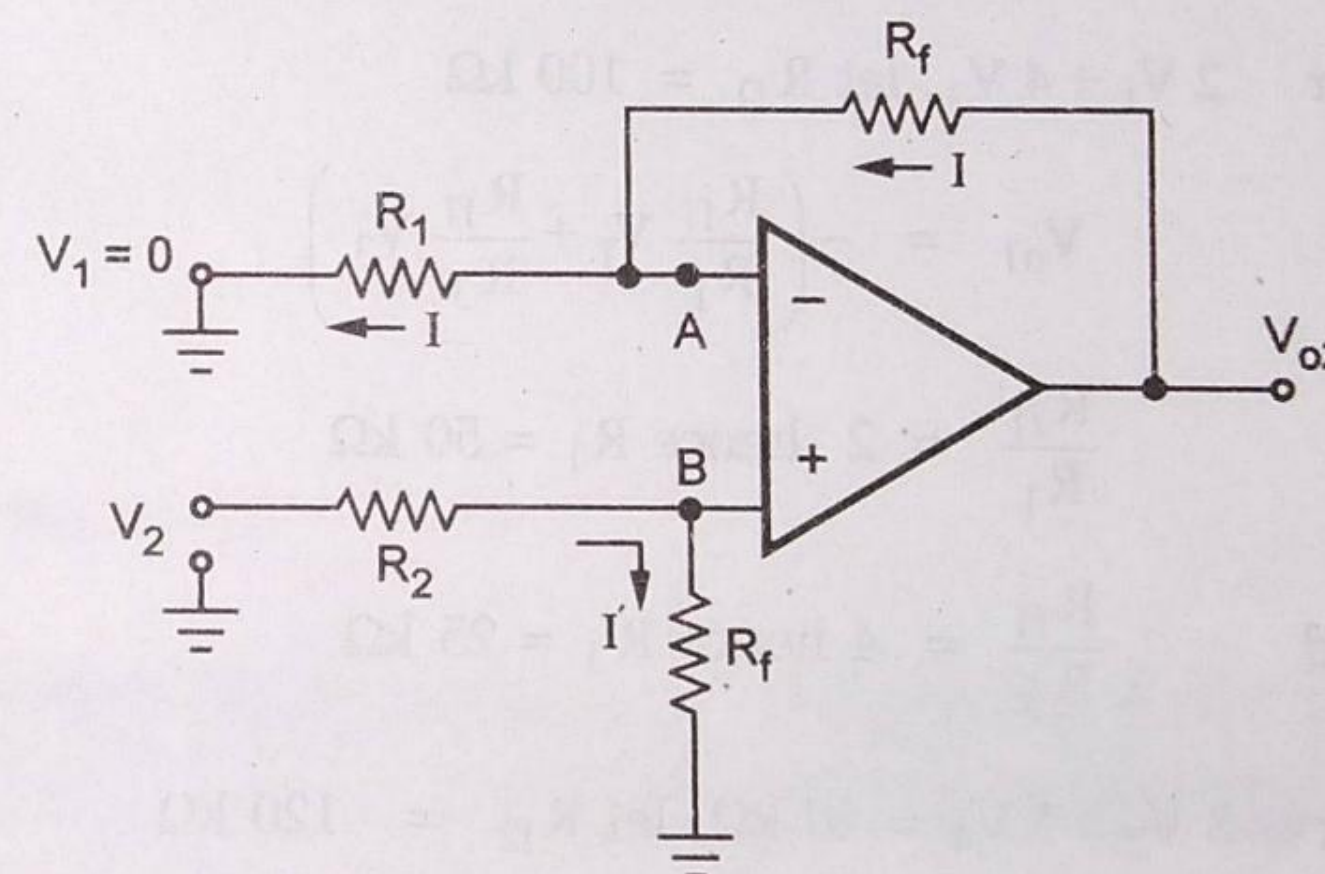

- Substituting  $V_B$  from (9.18.2) in (9.18.3) we get,

$$V_{o2} = \left[1 + \frac{R_f}{R_1}\right] \left[\frac{R_f}{R_2 + R_f}\right] V_2 \quad \dots (9.18.4)$$

- Hence using Superposition principle,  $V_o = V_{o1} + V_{o2}$

$$\therefore V_o = -\frac{R_f}{R_1} V_1 + \left[1 + \frac{R_f}{R_1}\right] \left[\frac{R_f}{R_2 + R_f}\right] V_2 \quad \dots (9.18.5)$$

- If the resistances are selected as  $R_1 = R_2$ ,

$$V_o = -\frac{R_f}{R_1} V_1 + \left[1 + \frac{R_f}{R_1}\right] \left[\frac{R_f}{R_1 + R_f}\right] V_2 = -\frac{R_f}{R_1} V_1 + \frac{R_f}{R_1} V_2$$

$$\therefore V_o = +\frac{R_f}{R_1} (V_2 - V_1) \quad \dots (9.18.6)$$

- Thus the output voltage is proportional to the difference between the two input voltages. Thus it acts as a subtractor or difference amplifier.

- If  $R_1 = R_2 = R_f$  is selected,

$$\therefore V_o = V_2 - V_1 \quad \dots (9.18.7)$$



**Fig. 9.18.4**

**Example 9.18.2** Find the output voltage of the following op-amp circuit shown in Fig. 9.18.5.

**APJAKTU : 2009-10, Marks 10**



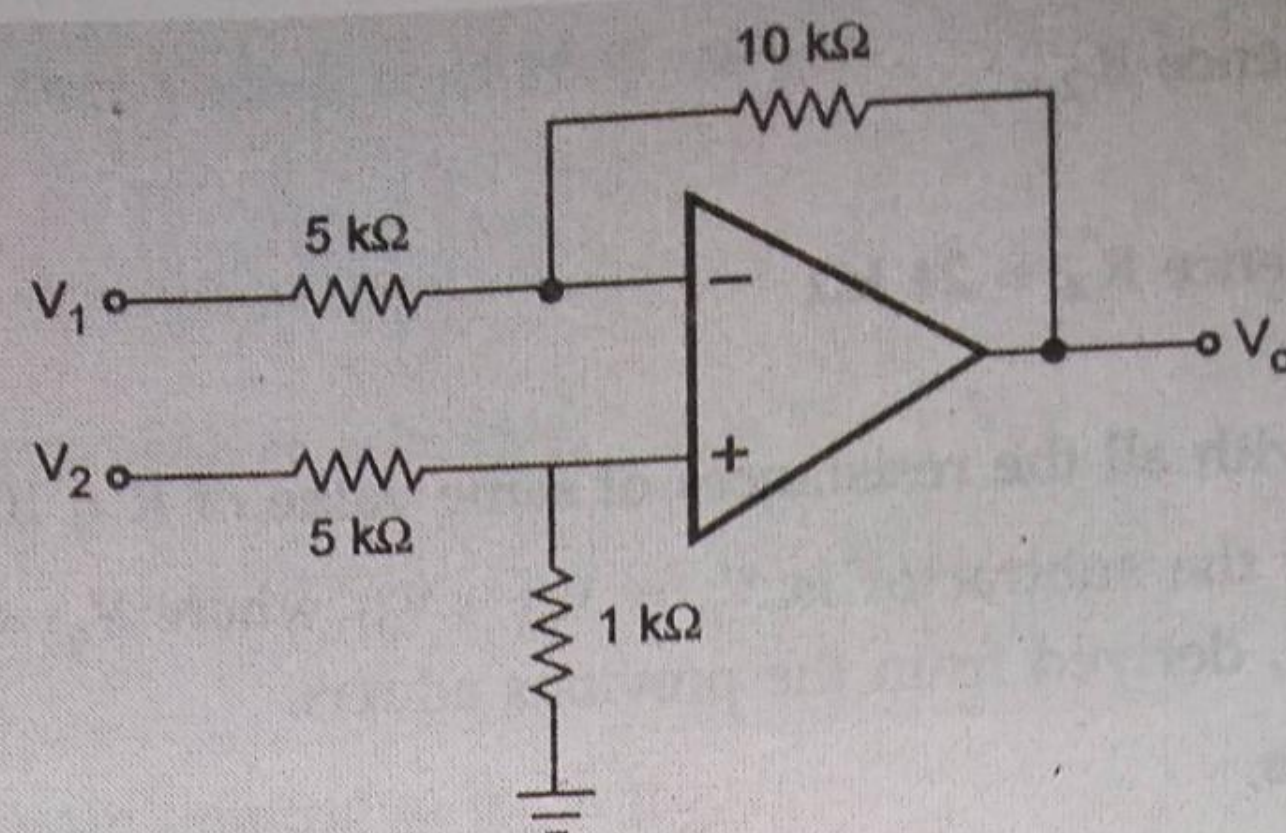


Fig. 9.18.5

**Solution :** Use Superposition principle.

**Case 1 :** Consider  $V_1$  alone,  $V_2$  is grounded.

The circuit acts as an inverting amplifier.

$$\begin{aligned}\therefore V_{o1} &= -\frac{10 \times 10^3}{5 \times 10^3} \times V_1 \\ &= -2V_1\end{aligned}$$

**Case 2 :** Consider  $V_2$  alone,  $V_1$  is grounded.

The circuit acts as non-inverting amplifier.

$$\begin{aligned}\therefore V_{o2} &= \left(1 + \frac{10 \times 10^3}{5 \times 10^3}\right) V_B \\ &= 3V_B\end{aligned}$$

$$\begin{aligned}\text{But } V_B &= \frac{V_2}{(5 \times 10^3 + 1 \times 10^3)} \times 1 \times 10^3 \\ &= \frac{V_2}{6}\end{aligned}$$

$$\therefore V_{o2} = 3 \times \frac{V_2}{6} = 0.5V_2$$

$$\therefore V_o = V_{o1} + V_{o2} = -2V_1 + 0.5V_2$$

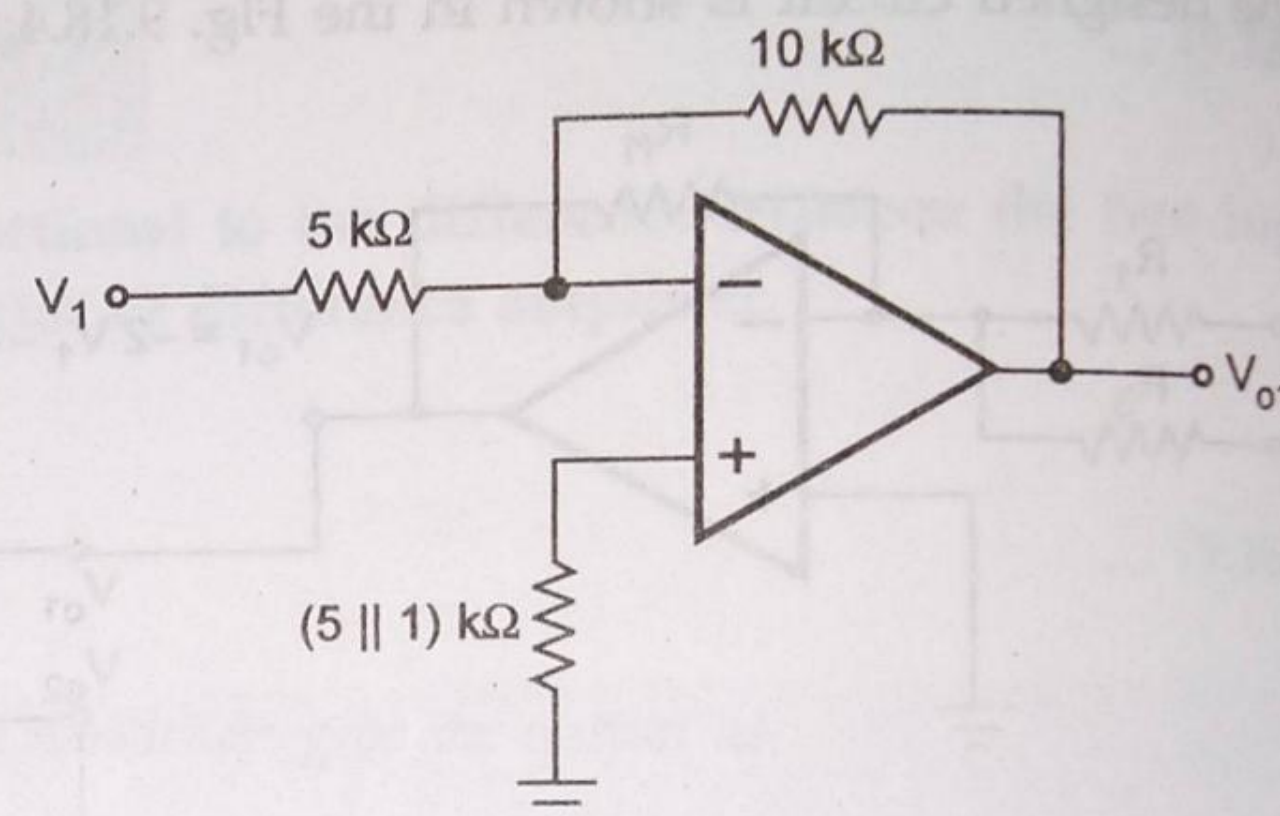


Fig. 9.18.5 (a)

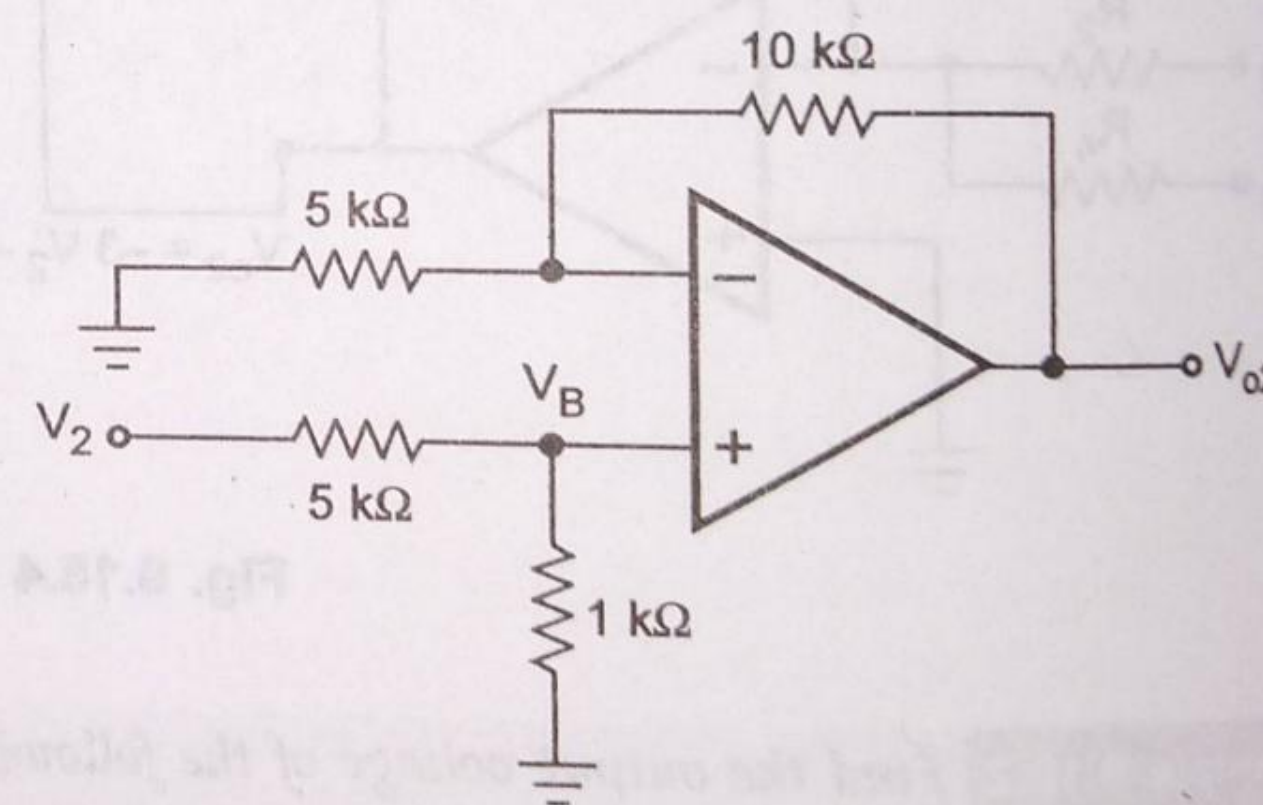


Fig. 9.18.5 (b)