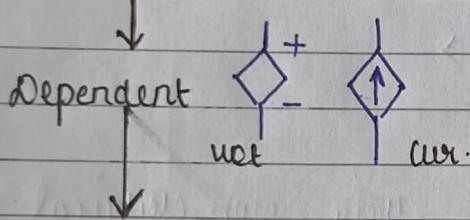


20/09/2022


## Electrical Sources

voltage source

current source



→ Dependent  
→ Independent

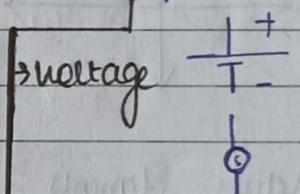

- voltage dependent voltage source  $V = kI_1$
- voltage dependent current source  $I = kV_1$
- current dependent voltage source  $V = kI_1$
- current dependent current source  $I = kV_1$


## Parameters / Elements

1) Resistance :  $(R) = \frac{P}{A}$

- 2) Inductance ( $L$ ) : Inductor stores energy in the form of magnetic energy field
- 3) Capacitance ( $C$ ) : Energy will be stored in the form of charge / electrical field.


## \* Properties

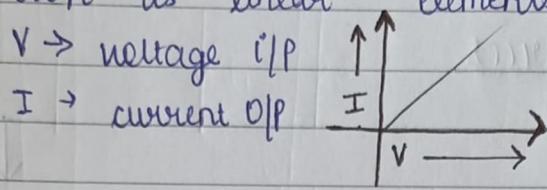1) linear  $\rightarrow$  The elements who follow the Ohm's law are known as linear elements



$V \rightarrow$  voltage i/p       $I \rightarrow$  current o/p      VI characteristic Representing a line then it is linear eq:- Resistance

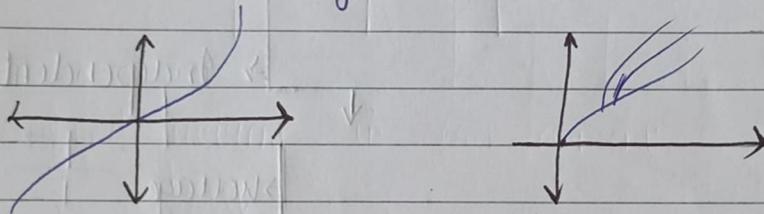2) Non-linear  $\rightarrow$  The elements who don't follow the Ohm's law  
\* Elements having curvilinear characteristics of VI



3) Active Elements : those elements having their own electrical energy

Passive Elements : Elements that do not have their own energy & works on behalf of the source

## Distributed Parameters

Those parameters which are distributed across length area

eg :- Rheostat

• open circuit

- there will be no current
- voltage may be there

• short circuit

- voltage is 0
- infinite current

## Dumped Parameters

Those parameters that are focused or concentrated on a specific point

Eg:- Resistance / Capacitance

## • Unilateral Elements

Elements that work in a specific direction eg: diode


## • Bilateral Elements - Elements

that work in a both direction


Eg: Resistance, induction

$\Rightarrow$  In a circuit (Active)

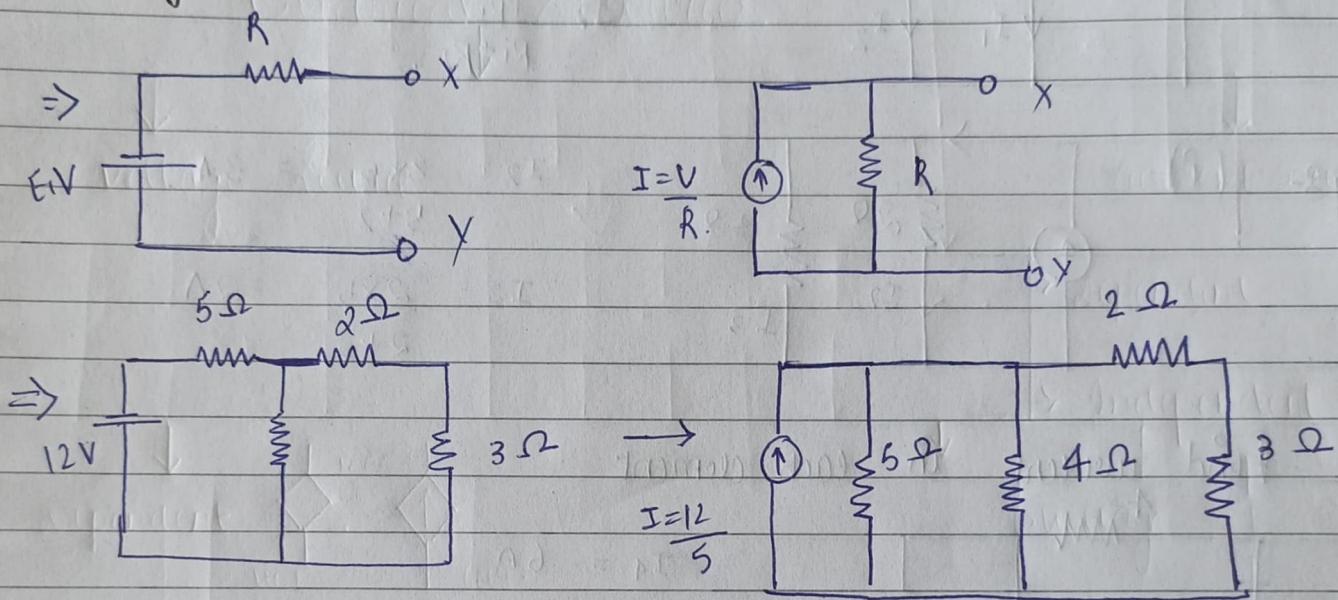
- Voltage Source to Current Source Conversion



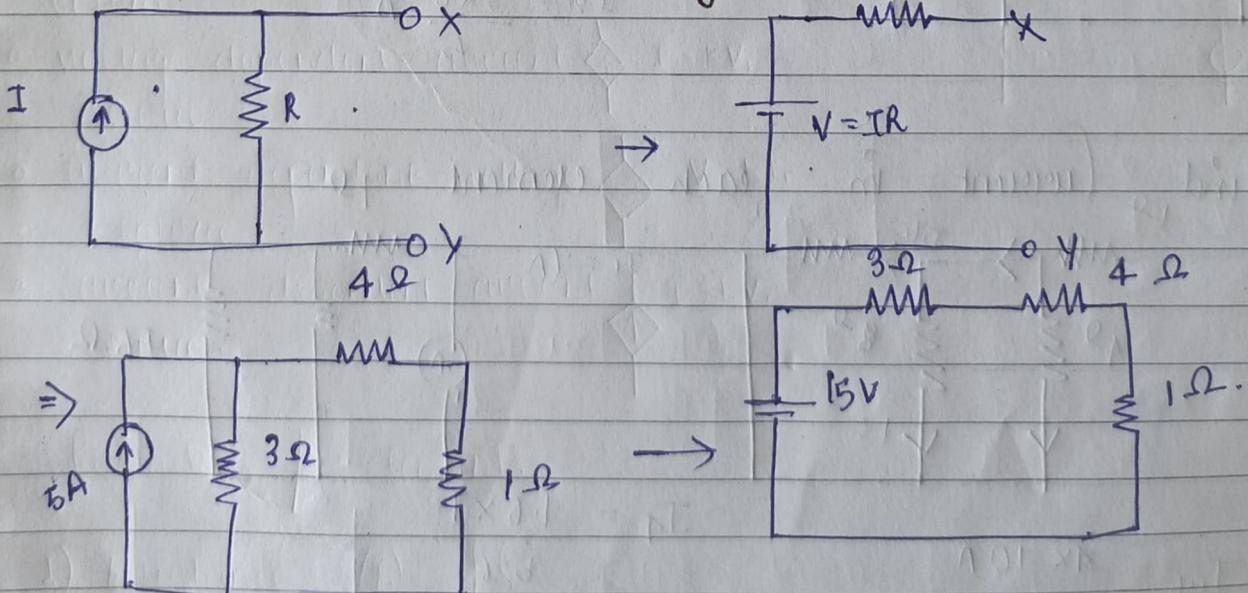- Current Source to Voltage Source Conversion




\* Current division Rule :-

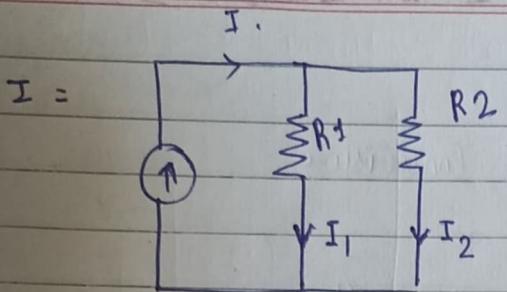

$$I_1 = \frac{IR_2}{R_1 + R_2}$$


$$I_2 = \frac{IR_1}{R_1 + R_2}$$

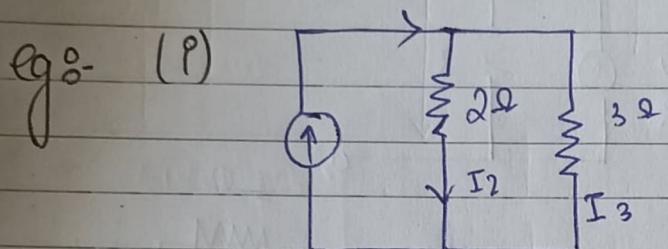

$$I_2 = \frac{3 \times 5}{5+2} = 3A$$

$$I_3 = \frac{2 \times 5}{2+3} = 2A$$

(ii) Find current in each element

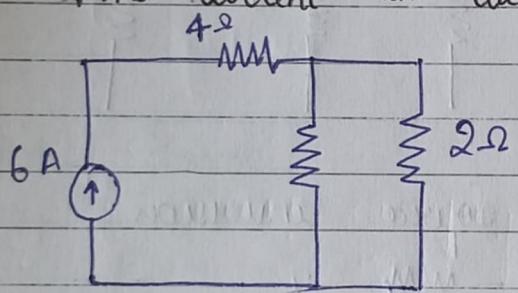


$$I_4 = 6A$$


$$I_3 = \frac{2 \times 6}{5} A$$

$$I_2 = \frac{3 \times 6}{5} A$$

(iii) Find current in each element

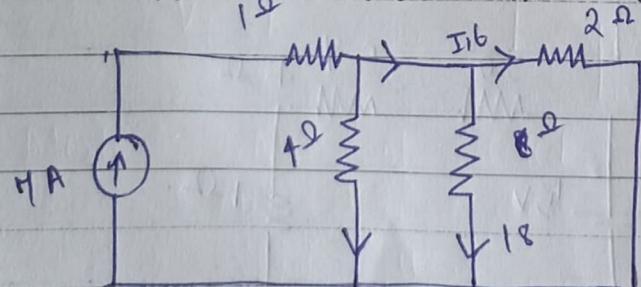

$$I_1 = 4A$$

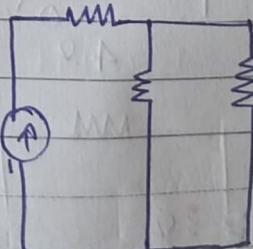

$$I_{1.6} = \frac{4 \times 70}{5.6^2} A$$

$$I_{1.6} = 5A$$

$$I_8 = \frac{I_{1.6} \times 2}{8+2}$$

$$I_8 = \frac{5 \times 2}{10} = 1A$$



$$I_4 = \frac{1.6 \times 7}{5.6} A$$

$$I_4 = 2A$$

$$I_2 = \frac{I_{1.6} \times 8}{8+2}$$

$$= \frac{5 \times 8}{10} = 4A$$

Q8) find current in each element.

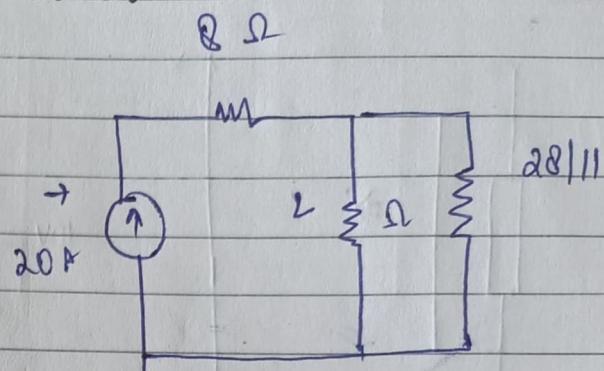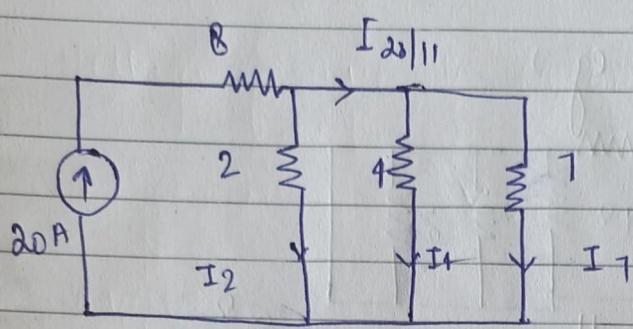

$$I_{28/11} = \frac{2 \times 20}{(22 + 28)/11}$$

$$= \frac{40 \times 11}{50}$$

$$I_4 = \frac{I_{28/11} \times 7}{11} = \frac{4 \times 11 \times 7}{5 \times 11}$$

$$= \frac{28}{5} A$$

$$I_4 = \frac{I_{20/11} \times 4}{11}$$


$$\Rightarrow \frac{4 \times 11 \times 4}{5 \times 11}$$

$$\Rightarrow \frac{16}{5} A$$

$$I_2 = \frac{20 \times 20}{(22 + 28)/11}$$

$$\Rightarrow \frac{20 \times 20}{50} = I_2 \quad \frac{56}{5} A$$

## \* Short Circuit Condition

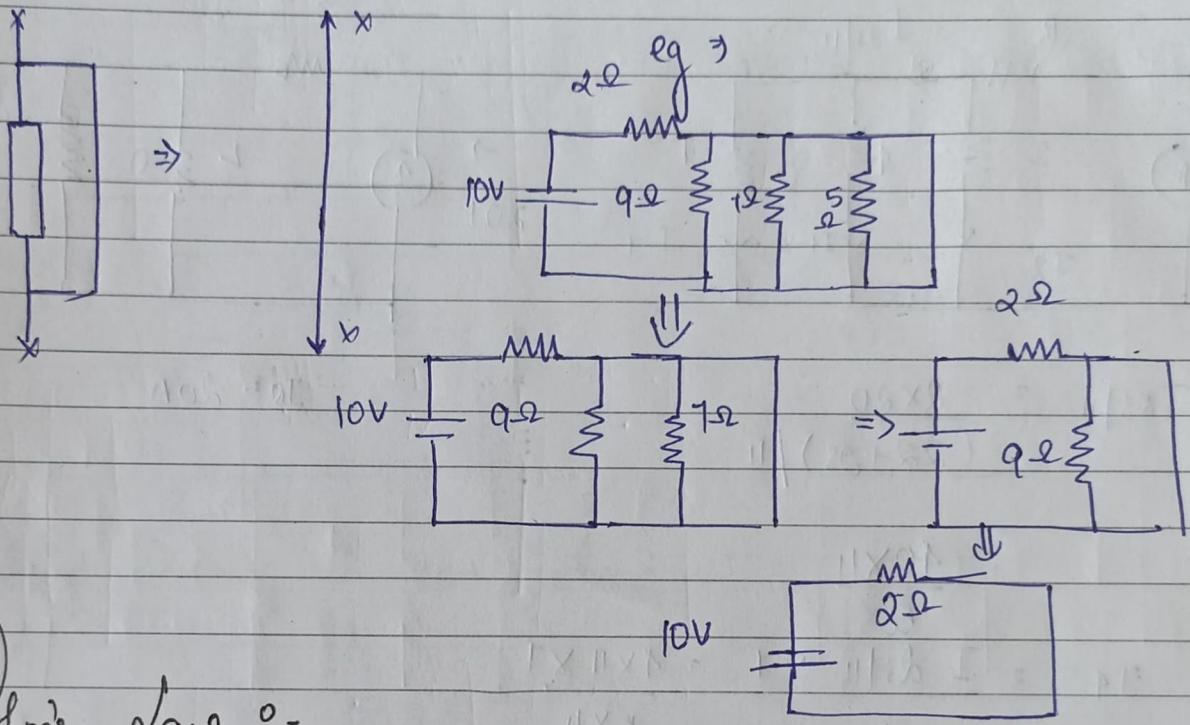


(Q) Ohm's law :-

If any current carrying conductor has its physical conditions constant then the current will be proportional to voltage

$$I \propto V$$

$$V = IR$$

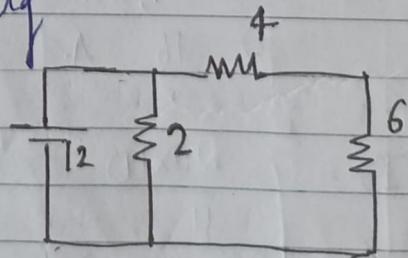Mesh :- No. of closed path having other closed path within it




loop Total No. of closed path present

Kirchoff's law

$$V = V_1 + V_2 + V_3$$



$$V = V_1 + V_2 + V_3 = 0$$

$$\therefore V = 0$$

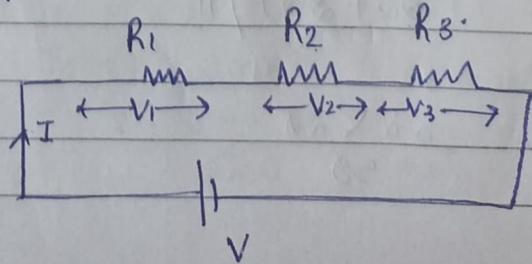

KCL



## Node / Junction

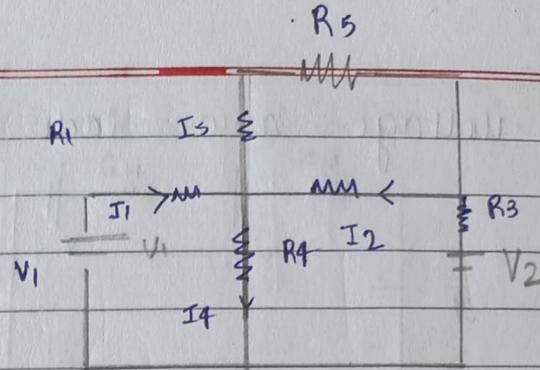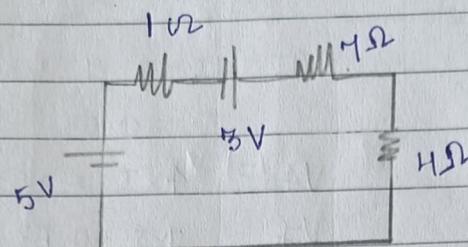

$$I_1 + I_2 = I_3 + I_4$$

$$I_1 + I_2 - I_3 - I_4 = 0$$


$$\sum I = 0$$

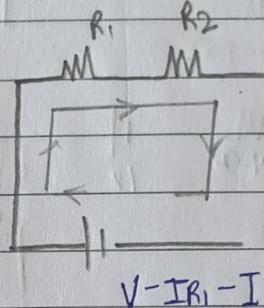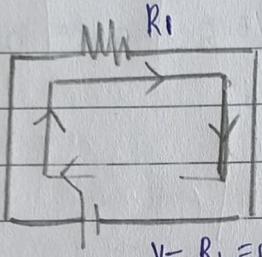

- For battery conditions if we are moving from -ve terminal to +ve terminal it will be taken as + sign. if we are moving from +ve to -ve terminal it will be taken as -ve sign.

- In a closed path if we assume specific direction & we are moving in the same direction voltage drops will be taken as -ve sign. If we are moving to the specified direction of the current it will be taken as +ve sign.

Find the voltage across each element.

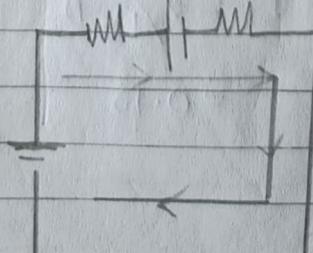

$$V_2 = \frac{2}{3} \times 2 = \frac{4}{3} V = 1.33V$$

$$V_1 = \frac{2}{3} V = 0.66V$$

$$+4 - 2I - 2 - I \times 1 = 0$$

$$2 = 3I$$


$$I = 0.66$$

$$I = \frac{2}{3}$$

$$V_2 = 2 \times I \\ = 2 \times 0.66 \\ \Rightarrow$$

Find Voltage across each element

①

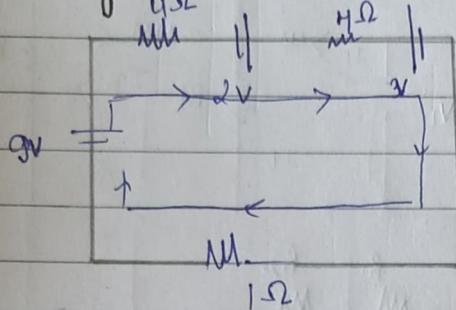

$$+9I - 4I + 2 - 3I - 3 - 5I = 0$$


$$I = 0.53$$

$$V_4 = 4 \times I = 0.53 \times 4 =$$

$$V_7 = 3 \times I = 0.53 \times 7 =$$

$$V_5 = 5 \times I = 0.53 \times 5 =$$

2)

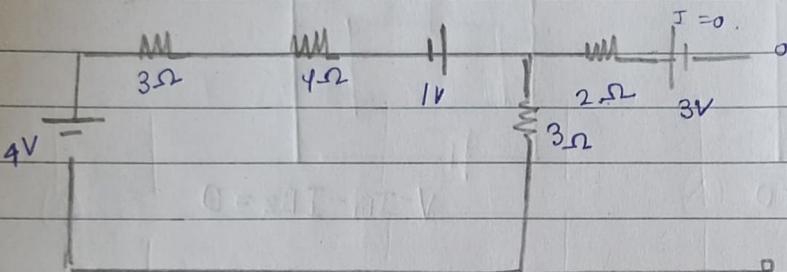

$$+4 - 3I_1 - 4I_1 + 1 = 3I = 0$$

$$I_1 = 0.54$$


$$V_A + 3 - 2 \times 0 - 3I_1 = V_B$$

$$V_A - V_B = -1.5$$

$$V_{AB} = -1.5$$

3) Find voltage across kernel A & B

⑤

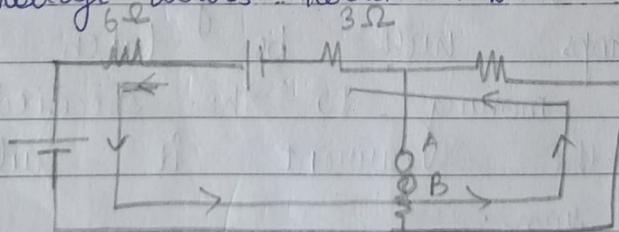

$$\Rightarrow -6I_1 - 5 - 2I_1 - 3I_1 = 0$$

$$7 - 6I_1 - 5 - 2I_1 - 3I_1 = 0$$

$$-11I_1 = 0$$

$$\Rightarrow I_1 = 0.18$$

$$I_1 = 2/11 \text{ A}$$


$$= 0.18$$

$$V_A + 2I_1 - 3 \times 0 = V_B$$

$$V_A - V_B = -3.6$$

$$V_{AB} = -3.6 \text{ V}$$

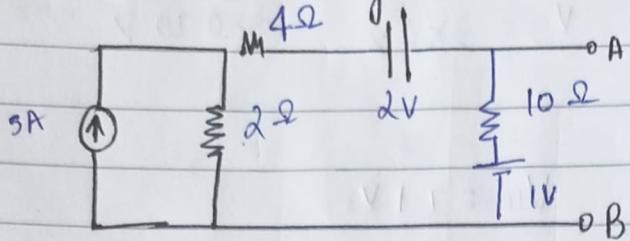find the Voltage across the terminal A & B



$$10 - 2I - 4I + 2 - 10I - 1 = 0$$

$$11 = 16I$$

$$I = \frac{11}{16} \text{ A} = 0.68 \text{ A}$$


$$V_A = 10I = 1 = V_B$$

$$V_A - V_B = \frac{1}{16} + 110 = \frac{126}{16}$$

$$\boxed{V_{AB} = 7.8 \text{ V}}$$

When we are working with different circuits then there are more current values which comes with the same sign. When calculated the circuit of same sign.

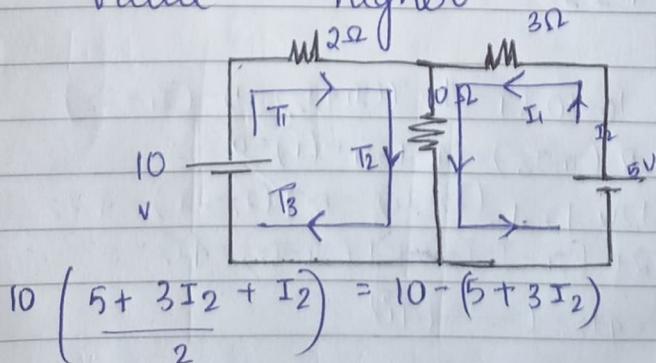When an element is common to mesh in which mesh we are moving we will take its value higher.



$$10 \left( \frac{5 + 3I_2 + I_2}{2} \right) = 10 - (5 + 3I_2)$$

$$25 + 5I_2 + 10I_2 = 10 - 5 - 3I_2$$

$$20I_2 = -20 \Rightarrow I_2 = -\frac{20}{20} = -0.7 \text{ A}$$

$$10 - 2I_1 - 10(I_2 + I_2) = 0$$

$$5 - 5I_2 - 10(I_1 + I_2) = 0$$


$$5 - 3I_2 = 10 - 2I_1$$

$$2I_1 - 3I_2 = 5$$

$$2I_1 = 5 + 3I_2$$

$$2I_1 = 5 - 3(0.7)$$

$$I_1 = 1.45 \text{ V}$$

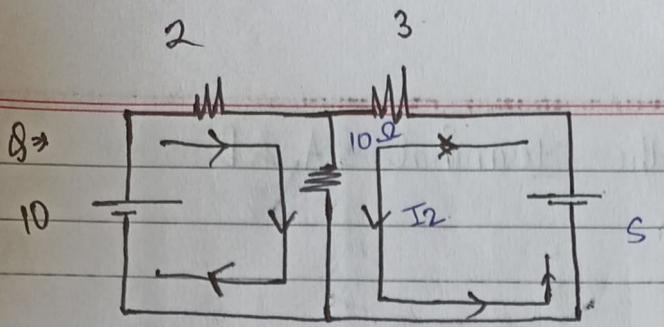


$$V_2 = 2 \times I_1 \Rightarrow 2 \times 1 \cdot 4 = 8V$$

$$V_3 = 3 \times I_2 \quad 3 \times 0 \cdot 10 = 30V$$

$$V_{10} = 7.1V$$

$$1.41 \downarrow \uparrow 1.40$$
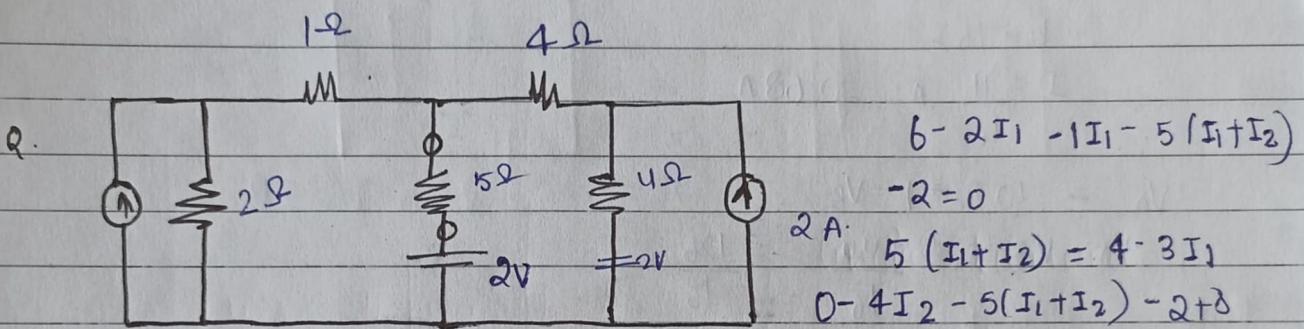
$$V_2 \Rightarrow 2 \times I_1 = 2 \times 1.41V$$



$$6 - 2I_1 - 1I_1 - 5(I_1 + I_2)$$

$$-2 = 0$$

$$2A: 5(I_1 + I_2) = 4 \cdot 3I_1$$

$$0 - 4I_2 - 5(I_1 + I_2) - 2 + 8$$

$$-4I_2 = 0$$

$$5(I_1 + I_2) = 6 - 8I_2$$

$$4 - 3I_1 = 6 - 8I_2$$

$$8I_2 - 2 = 3I_1$$

$$8 \times 0.35 - 2 = 3I_1$$

$$2.8 - 2 = 3I_1$$

$$I_1 = 0.8/3$$

$$0.27$$

$$5 \left[ \frac{8I_2 - 2 + I_2}{3} \right] = 4 - [8I_2 - 2]$$


$$5 - (8I_2 - 2 + 3I_2) = 12 - 24I_2 + 6$$

$$55I_2 - 10 = 12 - 24I_2 + 6$$

$$79I_2 = 28$$

$$I_2 = 28/79 = 0.35$$
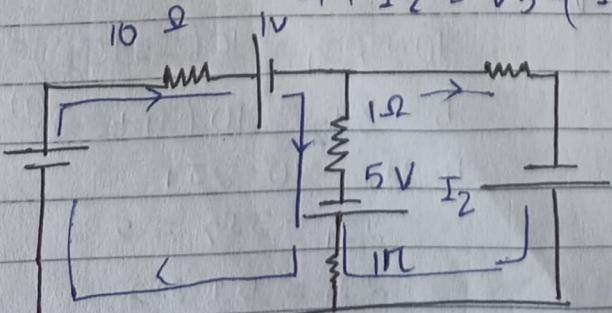
$$I_1 + I_2 = V_5 = (I_1 * I_2) \times 5$$



$$10 - 10I_1 - 1 - 7(I_1 + I_2) + 5 - (I_1 - I_2)$$

$$8(I_1 - I_2) = 14 - 10I_1 - (i) = 0$$

$$12V \cdot 12 - 1(I_2 - I_1) - 5 - 7(I_2 - I_1) - 4I_2$$

$$12 + (I_1 - I_2) - 5 + 7(I_1 - I_2) - 4I_2 = 0$$


$$8(I_1 - I_2) = 4I_2 - 7 \quad (ii)$$

$$I_1 = 1.476A$$
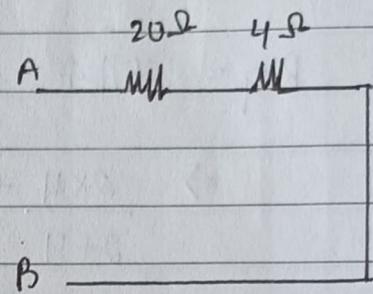
## Equivalent Resistance

$$R_{AB} = R_{eq}$$

$$\begin{aligned} R_{eq} &= R_1 + R_2 \\ &= 20 + 4 \\ &= 24 \end{aligned}$$




$$\begin{aligned} R_{eq} &= 9 + \frac{4}{9} \\ &= 3 + \frac{4 \times 9}{4+9} \end{aligned}$$

$$\Rightarrow 3 + \frac{36}{13}$$

$$\Rightarrow \frac{39 + 36}{13}$$

$$= \frac{75}{13}$$

$$= 5.76$$

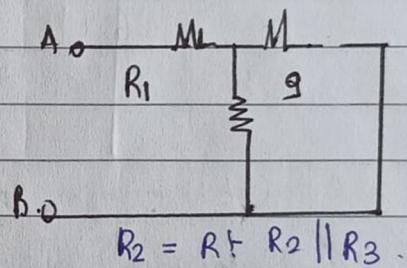


$$R_{eq} = R_1 + R_2 + R_3$$

$$R_{eq} = 2 + \frac{6 \times 7}{13} = 2 + \frac{42}{13}$$

$$\Rightarrow 2 + 3.23$$

$$= 5.23 \Omega$$

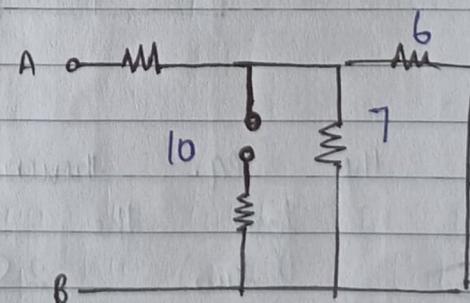


Q)

$$\text{Req} = 2 \parallel 4 + 9 \parallel 7$$

$$\Rightarrow \frac{2 \times 4}{2+4} + \frac{9 \times 7}{9+7}$$

$$\Rightarrow \frac{8}{6} + \frac{63}{16}$$

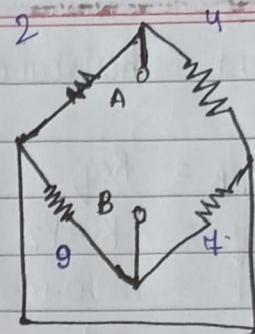
$$\Rightarrow \frac{64 + 108}{48} \Rightarrow \frac{172}{48}$$



$$= 5.2$$


lineare bilateral

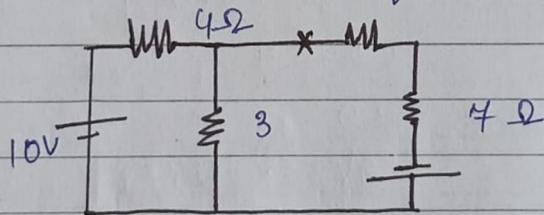$\Rightarrow$  Thévenin's theorem - A complex active, single input voltage source connected with load.



Q) Find the eq. Thévenin's circuit, Thévenin's theorem for the calculation of current in (two)  $2\Omega$  resistance

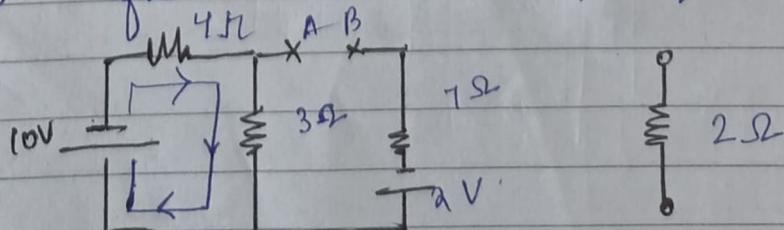Step 1 Remove the element across which we have to find the current / eq. circuit.



Step - 2

Calculate the voltage across the open terminals & this voltage which will called Themonius voltage

$$V_{AB} \Rightarrow 10 - 4I - 3I = 0$$

$$10 = 4I$$

$$I = 10/4 \Rightarrow 1.4 A$$

$$V_{AB} \Rightarrow 6.2$$


$$V_{TH} = 6.2$$

Step - 3

1) Find the eq. resistance of the circuit obtained by steps & this eq. resistance will called Themonius eq. resistance or  $R_{TH}$ .

\* shot all the voltage circuit (if the internal resistance is given it will be exist)

2) Open all the current sources.

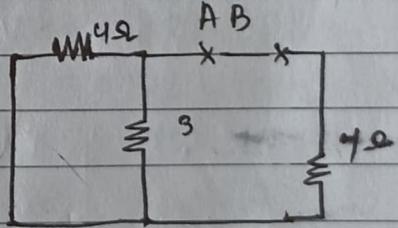


$$R_{TH} = 3||4 + 4$$

$$R_{TH} = \frac{3 \times 4}{3+4} + 4 \Omega$$



$$\Rightarrow 8.4 \Omega$$

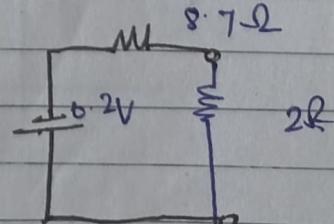Draw the circuit containing  $V_{TH}$  &  $R_{TH}$  in the circuit. Attach the element in the circuit which was removed in the step this circuit will called Themonius eq. circuit



$$I_{Th} = \left( \frac{6 \cdot 2}{8 \cdot 7 + 2} \right) A \Rightarrow$$

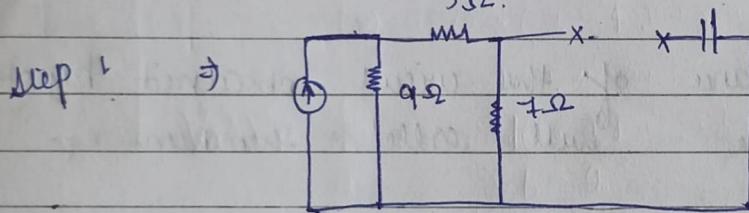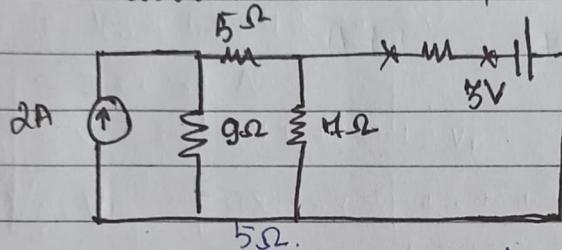Q) find the current in  $4\Omega$  of resistor in  
thermionic current



Step 2  $\Rightarrow$   $18 - 9I - 5I - 7I = 0$   
 $18 = 21I$

$$I = 0.85$$

$$V_A - 4I - 3 = V_B$$

$$V_A - V_B = 3 + 7I \div 3 + 7 \times 0.85$$

$$\Rightarrow -3 + 9.5$$


$$\Rightarrow 6.5$$

Step 3:  $R_{Th} = (5+9)\parallel 7$


$$\Rightarrow 14 \parallel 7$$

$$\Rightarrow \frac{14 \times 7}{14+7} \Rightarrow \frac{98}{21}$$

$$= 4.67$$

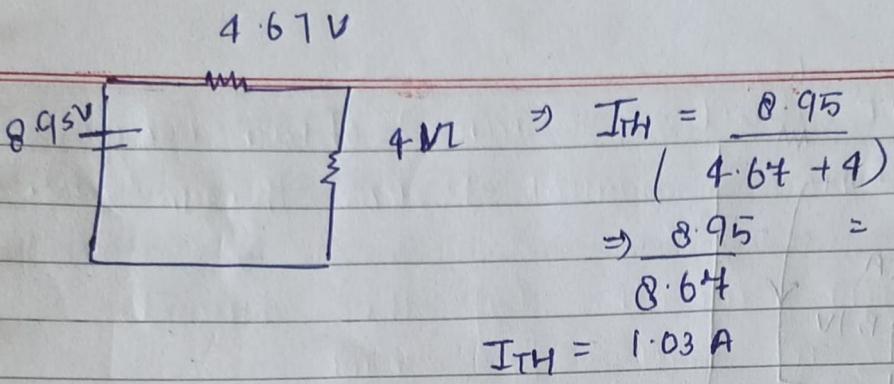

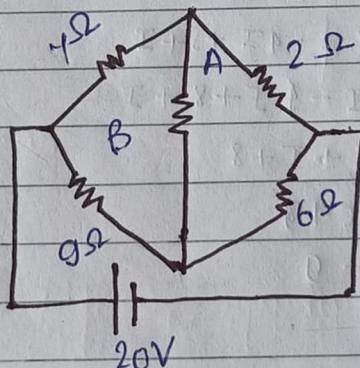Q.1) Find the current in 1Ω resistor using Thévenin's theorem.



$$V_A = 2I_1 + 6I_2 = V_B$$

$$V_A - V_B = 2I_1 - 6I_2$$

$$V_{TH} = 2 \times 2.2 - 6 \times 1.33$$

$$V_{TH} = 3.5 V$$

$$I_1 = \frac{20}{4+2} = \frac{20}{6} = 2.2$$


$$R_{TH} = 11/2 + 9/6$$


$$= \frac{1 \times 2}{1+2} + \frac{9 \times 6}{9+6}$$

$$I_2 = \frac{20}{9+6} = \frac{20}{15} = 1.33$$

$$\Rightarrow 4.26 \Omega$$

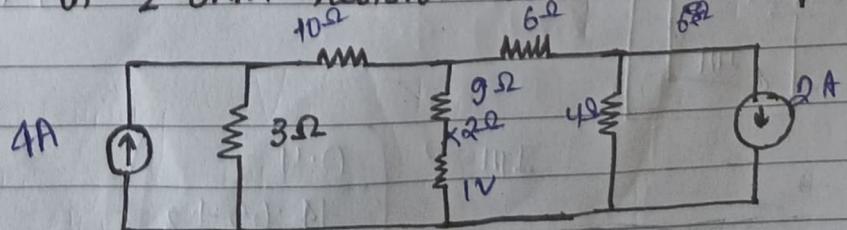Q.2) Find the current in 2 ohm resistor with the help of Thévenin theorem



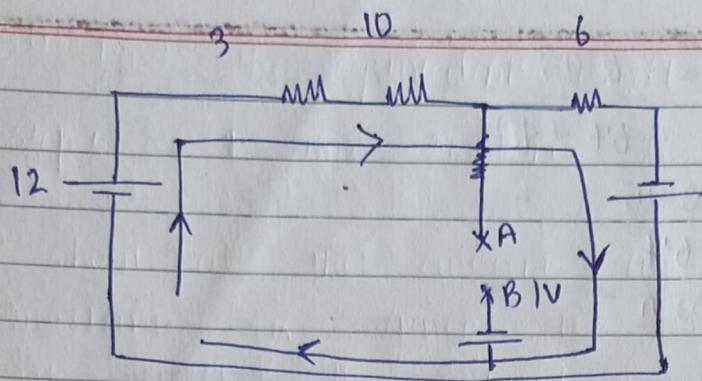

$$12 - 3I - 10I - 6I - 4I - 8 = 0$$

$$I = 0.86 \text{ A}$$

$$V_A - 9 \times 0 - 6I - 4I + 8 + I = V_B$$

$$V_A - V_B = -9 \times 0 - 6I - 4I + 8 + I$$

$$\Rightarrow 0 - 6I - 4I + 8 + I$$

$$\Rightarrow -10I + I + 8$$

$$V_A - V_B \Rightarrow -10I + 8$$

$$\Rightarrow 8 - 8$$

$$V_A - V_B \Rightarrow 0.4$$


$$V_{TH} = 4V$$

$$R_{TH} = 9 + 13 // 10$$

$$= 9 + \frac{13 \times 10}{13 + 10} \Rightarrow \frac{9}{1} + \frac{130}{23}$$

$$\Rightarrow \frac{207 + 130}{23} \Rightarrow \frac{337}{23}$$

$$= 14.65$$

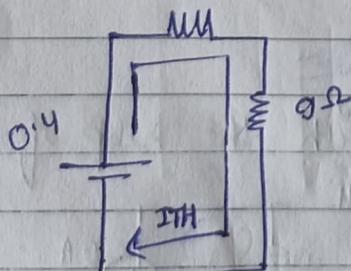


$$I_{TH} \Rightarrow \left( \frac{0.4}{14.65 + 2} \right) \Rightarrow \frac{0.4}{16.65}$$

$$\Rightarrow 0.02$$

Norton's Theorem :- A complex active linear bilateral circuit can be represented by a single voltage source connected with equivalent series resistance & load.

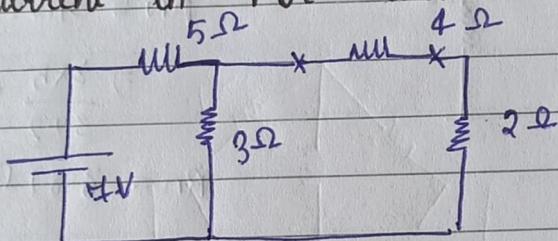
Find the current in  $4\Omega$  resistor in circuit using Norton's theorem




Step 1

Remove the element across which we have to find the current across eq. circuit

Step 2

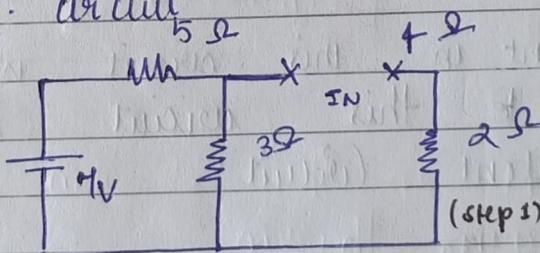

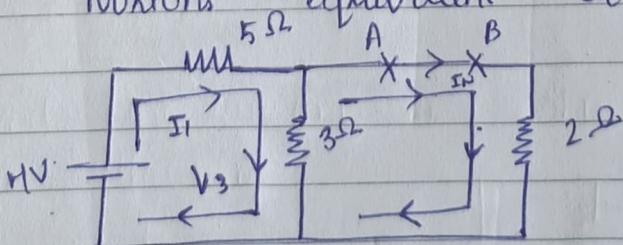Connect the / short the open terminals after step 1. & find the current in this branch it may called the Norton's equivalent current.



$$+12 - 5I_1 - 3(I_1 - I_2) = 0 \quad \text{--- (1)} \Rightarrow 4 - 5I_1 - 3I_1 + 3I_2 = 0$$

$$-2I_2 + 3(I_2 - I_1) = 0 \quad \text{--- (2)} \Rightarrow 2I_2 - 3I_2 + 3I_1 = 0$$

$$\underbrace{4 - 5I_1 - 3I_1}_{-8I_1} - 3I_1 + 3I_2 = 0 \quad \text{--- (3)} \Rightarrow 2I_2 - 3I_2 + 3I_1 = 0$$

$$-I_2 - 3I_1 = 0$$


$$4 - 8I_1 - 3I_2 = 0$$

$$4 - 8I_1 - 3 \times 3I_1 = 0$$

06/14

Norton's Theorem :- A complex active linear bilateral circuit can be represented by a single voltage source connected with equivalent series resistance & load.

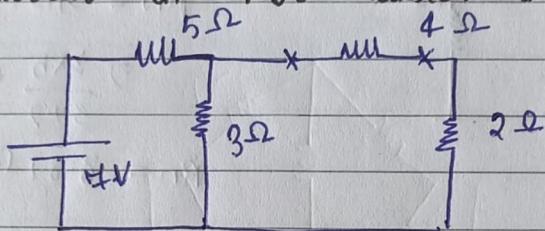
Find the current in  $4\Omega$  resistor in circuit using Norton's theorem




Step 1

Remove the element across which we have to find the current across eq. circuit

Step 2

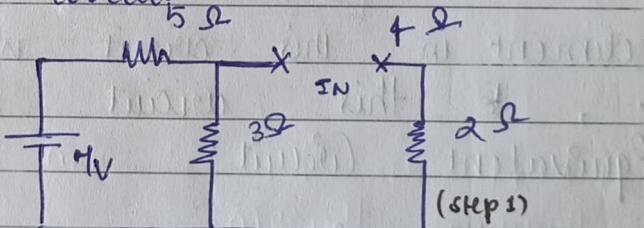

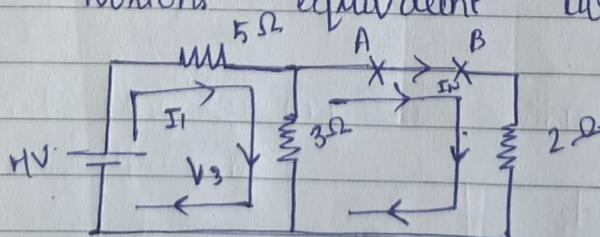Connect the / short the open terminals after step 1. & find the current in this branch it may called the Norton's equivalent current.



$$12 - 5I_1 - 3(I_1 - I_2) = 0 \quad \textcircled{1} \Rightarrow 12 - 5I_1 - 3I_1 - 3I_2 = 0$$

$$12 - 2I_2 - 3(I_2 - I_1) = 0 \quad \textcircled{2} \Rightarrow 12 - 2I_2 - 3I_2 + 3I_1 = 0$$

$$12 - 5I_1 - 3I_1 - 3I_2 = 0$$

$$12 - 2I_2 - 3I_2 - 3I_1 = 0$$

$$-I_2 - 3I_1 = 0$$

$$3I_1 = I_2$$

$$12 - 8I_1 - 3I_2 = 0$$

$$12 - 8I_1 - 3 \times 3I_1 = 0$$


$$12 - 8I_1 - 9I_1 = 0$$

0674

Q) Find the equivalent circuit (resistance) obtained by  
Step 1 & 2 this resistance is called Norton's theorem ( $R_N$ ).

$\Rightarrow$  short all the current circuit (if the internal  
resistance is given it will be exist)

Open all the current sources.

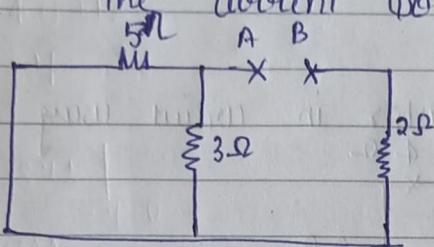

$$R_N = 3 \parallel 5 + 2$$


$$\Rightarrow \frac{3 \times 5}{3+5} + \frac{2}{1} \rightarrow \frac{15}{8} + 2$$

$$R_N = 3.81 \Omega$$

Q) Draw the circuit containing circuit  $I_N$  &  $R_N$  parallel

Attach the element in this circuit which was removed  
in step 1. If this circuit is called

Norton's Equivalent Circuit

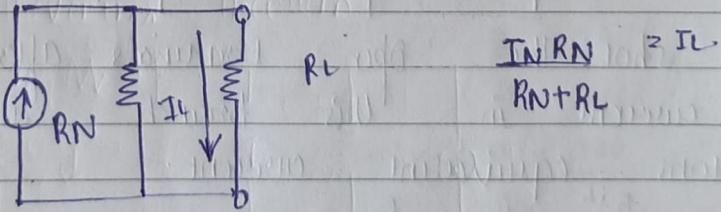


$$I_L \Rightarrow \frac{0.67 \times 8.81}{8.81 + 4}$$

$$\Rightarrow 0.32$$


$$\frac{I_N R_N}{R_N + R_L} = I_L$$

## ★ Numericals

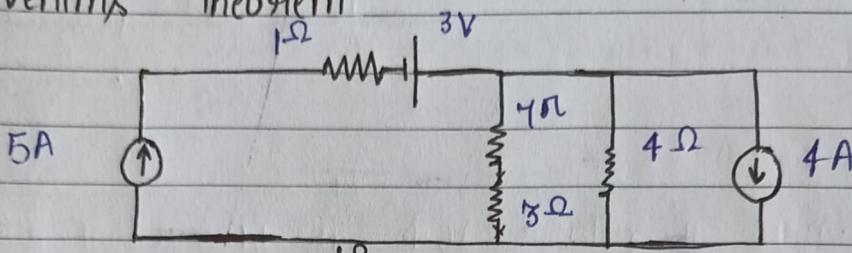1) Find the current in  $3\Omega$  register with the help of Thevenin's Theorem



Sol:-

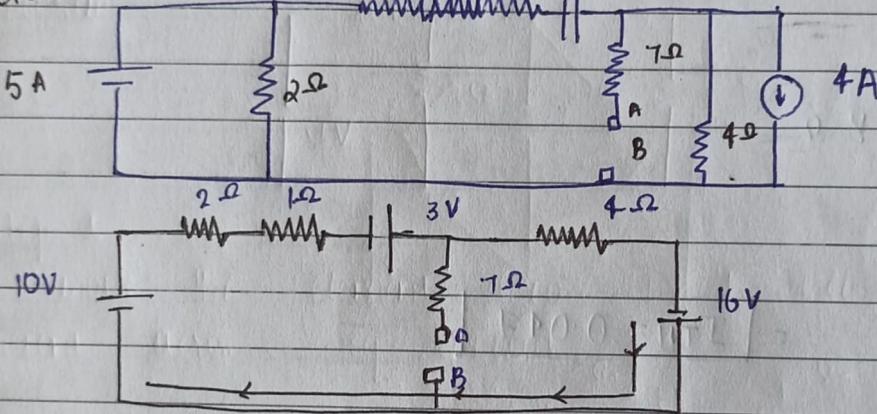

$$16 - 4I + 10 - 2I - 1I + 3 = 0$$

$$29 - 7I = 0$$

$$I = \frac{29}{7}$$

$$I = 4.14$$


$$V_A - 4 \times 0 + 16 - 4I = V_B$$

$$V_A - V_B = -16 + 4I$$

$$V_A - V_B = -16 + 4 \times 4.14$$

$$V_A - V_B = -0.56$$


$$V_{TH} = 0.56$$

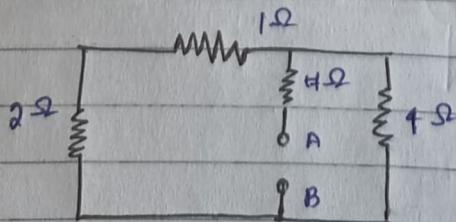

$$R_{TH} = 4 + 3 \parallel 4$$


$$R_{TH} = \frac{4 + 3 \times 4}{3+4}$$

$$R_{TH} = \frac{4 + 12}{4}$$

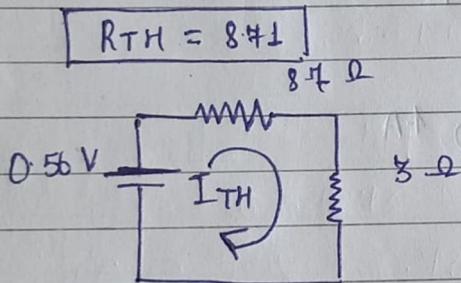

$$I_{TH} = \left( \frac{0.56}{8+3} \right) = I_{TH} = 0.047$$

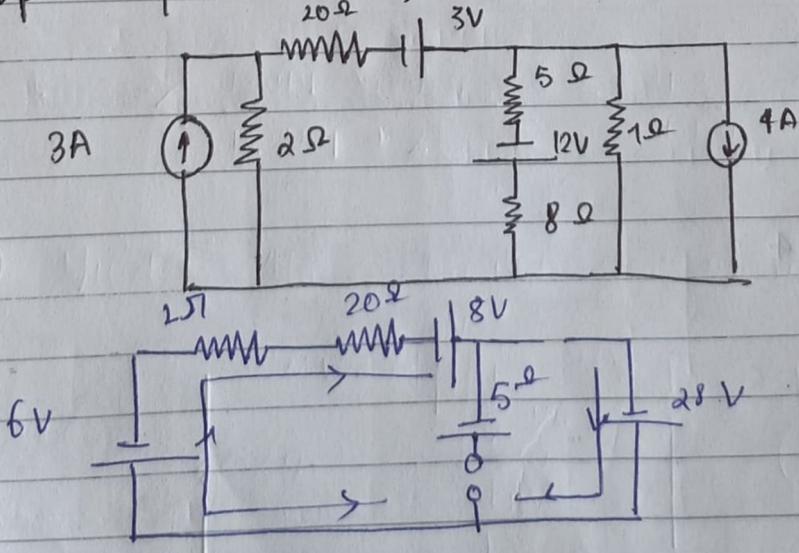2) Find the current in the 80 ohm resistor with the help of Thevenin's theorem



$$20 + 6 - 2I - 20I + 3 - 4I = 0$$

$$64 = 29I$$


$$I = \frac{34}{29} = 1.17$$

$$V_A + 12 - 4 \times I + 28 = V_B$$

$$V_A - V_B = -28 - 12 + 4 \times I$$

$$V_A - V_B = -40 + 4 \times 1.2 I$$

$$V_{TH} = 81.11$$

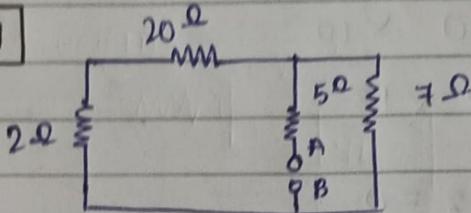


$$= 5 + 22/7$$

$$= 5 + 22 \times 1 \Rightarrow 5 + \frac{154}{29}$$

$$\Rightarrow \frac{145 + 154}{29}$$

$$= \frac{299}{29} = 10.31$$


$$R_{TH} = 10.31$$

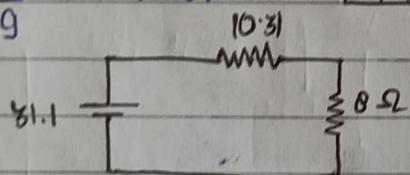


$$I_{TH} = \frac{V_{TH}}{R_{TH} + R}$$

$$I_{TH} = \frac{31.1}{10.31 + 8}$$

$$I_{TH} = 1.69$$

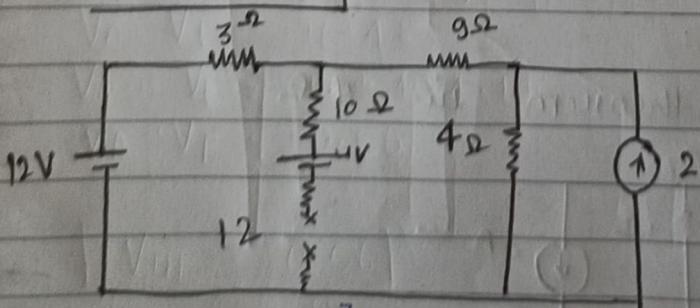

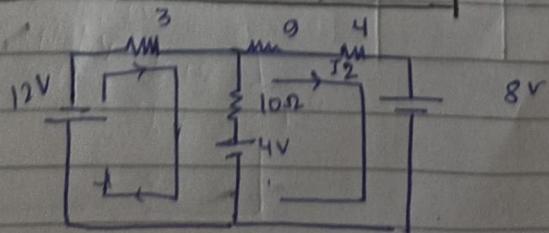Find the current in  
12Ω resistor by  
Norton's theorem.



$$12 - 3I_1 - 10(I_1 - I_2) - 4 = 0 \quad \text{--- (1)}$$

$$-9I_2 - 4I_2 - 8 + 4 - 10(I_2 - I_1) = 0 \quad \text{--- (2)}$$

$$8 - 18I_1 + 10I_2 = 0 \times 10$$

$$-4 + 10I_1 - 23I_2 = 10 \times 13$$

$$-80 - 130I_1 + 100I_2 = 0$$

$$\underline{-52 + 130I_1 - 299I_2 = 0}$$


$$28 - 199I_2 = 0$$

$$I_2 = \frac{28}{199} = 0.14$$

$$I_1 = 0.43$$

$$I_N = I_1 - I_2 = 0.43 - 0.14$$

$$= 0.59 \text{ A.}$$

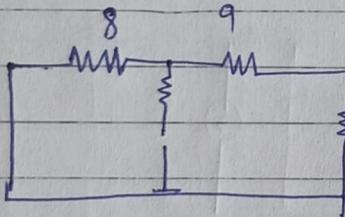


$$= R_N = \frac{10 + 13}{13 + 3}$$


$$\Rightarrow 10 + \frac{13 \times 3}{13 + 3} \Rightarrow 10 + \frac{39}{16}$$

$$\Rightarrow 12.4$$

$$I \Rightarrow \frac{12.44 \times 0.59}{12.44 + 2} = \frac{4.3}{14.4} \Rightarrow 0.3.$$

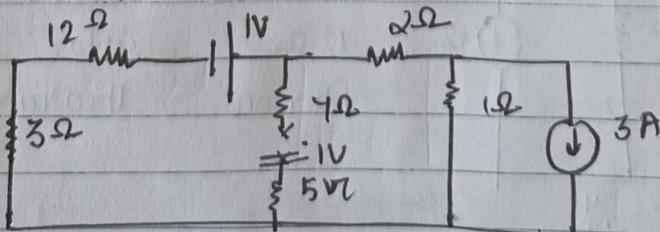Q) Find the Norton's theorem in  $4\Omega$



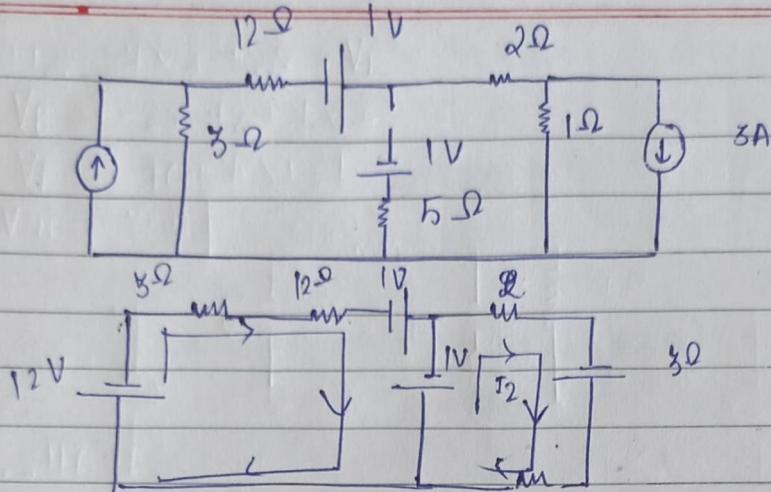

$$12 - 5I_1 - 12I_1 + 1 + 1 - 5(I_1 - I_2) = 0$$

$$-1 - 2I_2 + 3 - I_2 - 5(I_2 - I_1) = 0 \quad \text{--- (1)}$$

$$14 - 20I_1 + 5I_2 = 0$$

$$2 - 8I_2 + 5I_1 = 0$$

$$2 + 5I_1 - 8I_2 = 0$$

$$14 - 20I_1 + 5I_2 = 0$$

$$14 + 20I_1 - 5I_2 = 0$$


$$20 - 2I_2 = 0$$

$$I_2 = \frac{20}{21} = 0.476$$

$$I_1 = 0.76$$

$$I_N = I_1 - I_2 \\ = 0.76 - 0.476$$

$$I_N = 0.24$$

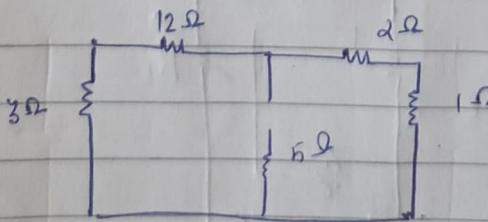

$$R_N = 5 + 3/15$$

$$\Rightarrow \frac{5 + 3 \times 15}{3 + 15}$$

$$R_N = 5 + \frac{45}{18}$$

$$\Rightarrow \frac{90 + 45}{18} = \frac{135}{18}$$

$$\Rightarrow 7.5$$

$$I_2 \Rightarrow \frac{0.04 \times 7.5}{7.5 + 1}$$


$$\Rightarrow \frac{0.300}{14.5}$$

$$\Rightarrow \frac{0.3}{14.5}$$


$$\Rightarrow 3/145$$

$$\Rightarrow 0.02 \text{ A}$$

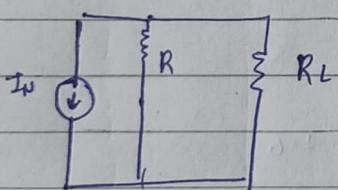Dual Property :- Norton's equivalent circuit change into Thevenin's equivalent circuit & Thevenin's equivalent circuit into Norton's equivalent circuit by source conversion.



$$I_{RN} = R_{TH} R_{TH}$$

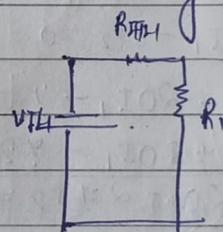


$$R_N = R_{TH}$$

Maximum Power Transfer form :-

$$P = \frac{E^2}{(R+R_L)}$$
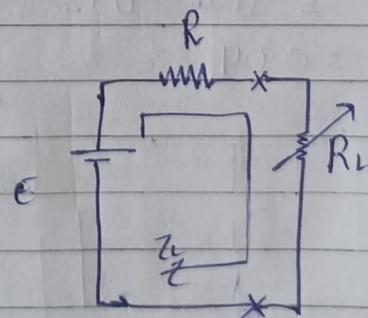
$$Power = I_L^2 R_L = \left[ \frac{E}{(R+R_L)} \right]^2 \times R_L$$



$$\frac{dP}{dR_L} = \frac{dP}{dR_L} \Rightarrow \left[ \frac{E^2 R_L}{(R+R_L)^2} \right]$$

$$Power = \left( \frac{E^2 + R_L}{R + R_L} \right)^2$$

$$\omega^2 = \left[ \frac{(R_1 + R_L)^2 \cdot \frac{d(R_1)}{dR_1} - R_L \frac{d}{dR_1} (R + R_L)^2}{(R + R_L)^4} \right]$$

$$E^2 \Rightarrow \left[ \frac{(R_1 + R_L)^2 \times 1 - 2R_L(R + R_L)}{(R_1 + R_L)^4} \right] = 0$$

$$E^2 = \left[ \frac{(R + R_L)^2 - 2R_L(R + R_L)}{(R + R_L)^4} \right] = 0$$

$$(R_1 + R_L)^2 - 2R_L(R_1 + R_2) = 0$$

$$(R_1 + R_L)^2 = 2R_L(R_1 + R_2)$$

$$\Rightarrow R = R_L$$

$$\frac{dP}{dR_1} = E^2 \left[ \frac{(R + R_L)^2 \times 1 - 2R_L(R + R_L)}{(R_1 + R_2)^4} \right]$$

$$\Rightarrow E^2 \Rightarrow \left[ \frac{R^2 + R_L^2 + 2RR_L - 2R_LR - 2R^3}{(R + R_L)^4} \right]$$

$$\Rightarrow \frac{dP}{dR_L} = E^2 \left[ \frac{R_2 - R_1^2}{(R + R_L)^4} \right]$$

$$\Rightarrow \frac{d}{dR_L} = \frac{dP}{dR_L} = \frac{d}{dR_L} \left[ \frac{E^2 (R^2 - R_L^2)}{(R + R_L)^4} \right]$$

$$\Rightarrow \omega^2 \left[ \frac{(R_1 + R_2)^4 \times -2RL - (R^2 - R_L^2) \times 4 \times (R + R_L)^3}{R + R_L} \right]$$

$$R_L = R$$

$$\frac{d^2P}{dR^2L} = -ve$$


$$P = \frac{E^2}{(R_1 + R_L)^2} R_L \Rightarrow \frac{E^2 \times R}{(R+R)^2} = \frac{E^2 R}{4R^2}$$

$$P_{max} = \frac{E^2}{4R}$$


$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

In a active linear bilateral circuit max. power will occur when low resistance is equivalent to total internal resistance of the circuit excluding load resistance.

Max. power occur is 50% in a circuit.

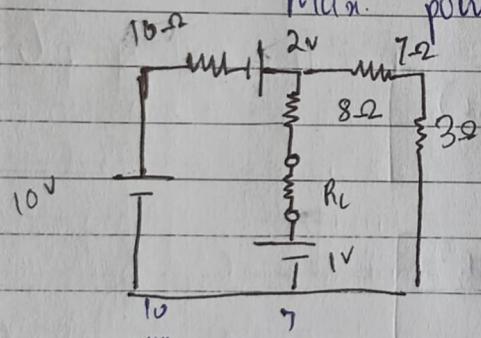

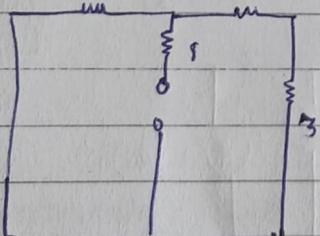What will be the value of  $R_L$  in shown circuit for the max power occurrence & also calculate max power across this.



$$R_L = 8 + 10 // 10 \\ \Rightarrow 8 + \frac{10 \times 10}{10 + 10}$$

$$R_L = 13\Omega$$

$$10 - 10I + 2 - 7I - 3I = 0$$

$$V_A = -8 \times 0 - 7I - 3I + 1 = V_B$$

$$12 = 20I$$


$$I = 0.6$$

$$V_A - V_B = 10I - 1$$

$$= 6 - 1$$

$$V_{TH} = 5V$$

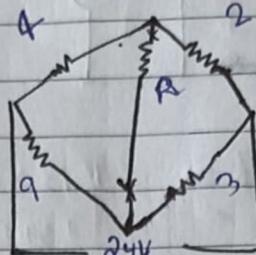Find the value of  $R$  in the shown circuit for the max. transfer theorem & also calculate Max. power.



$$R_{eq} \Rightarrow 4//2 + 9//3 \\ \Rightarrow \frac{4 \times 2}{4+2} + \frac{9 \times 3}{9+3} \Rightarrow \frac{8}{6} + \frac{27}{12} \Rightarrow \frac{16+21}{12} \Rightarrow \frac{43}{12}$$

$$\Rightarrow \frac{43}{12} = 3.58$$

$$R_L = 3.58$$

$$I_1 \frac{24V}{4+2} = \frac{24}{6} = 4A \quad I_2 \quad \frac{24}{9+3} \Rightarrow \frac{24}{12} = 2A$$

$$V_A - 2I_1 + 3I_2 = V_B$$

$$V_A - V_B = +2I_1 - 3I_2$$


$$\Rightarrow 2 \times 4 - 3 \times 2$$

$$\Rightarrow 8 - 6$$

$$V_{TH} = 2V$$


$$P_{max} = \frac{E^2}{4R} \Rightarrow \underline{(2)}$$

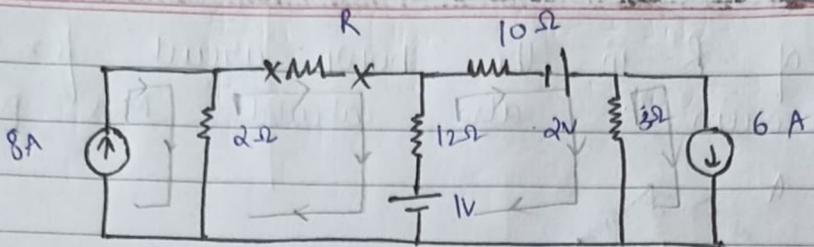Find the value of  $R$  for Max. Power transfer theorem & also calculate the Max. Power



$$R = \frac{R + (13 \times 12)}{13 + 12} = 8.24 \Omega$$

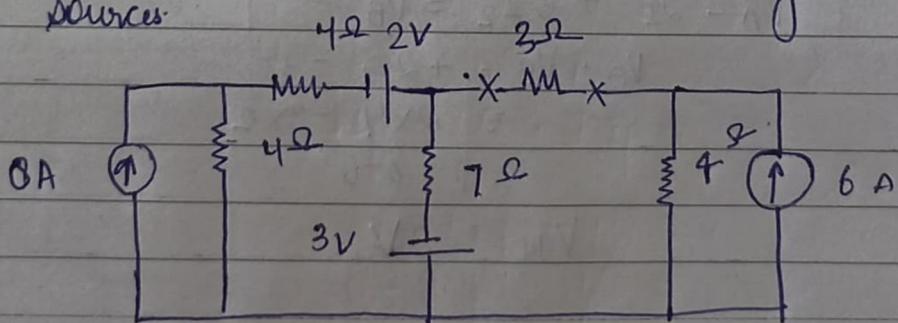
Superposition Theorem - In a active linear bilateral network the superposition theorem is used for the calculation of a current in a specific element by the summing of (Algebraic) individual current by diff sources.



Calculate the current in 3Ω resistor in 3Ω Resistor  
Step 1. Mark all the sources with specific number 1, 2 & 3

Step 2. Take source 1 & remove other sources to calculate the current in specific element

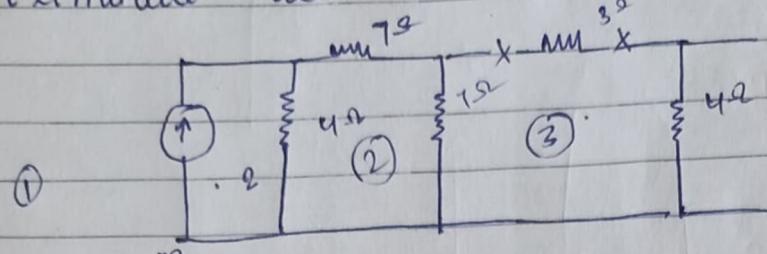Eliminate all the other sources in except 1.




$$4 \parallel 7 \Rightarrow \frac{4 \times 7}{4+7} = \frac{4}{11} = 0.36 \text{ A}$$

$$I_0 \Rightarrow \frac{8 \times 4}{10.5 + 4} = \frac{32}{14.5} = 2.20 \text{ A}$$

$$I_x = \frac{2.20 \times 4}{4+4} = \frac{8.80}{8} = 1.10 \text{ A}$$

Due to source 1 current in 3 ohm resistor is  $1.10 \text{ A}$

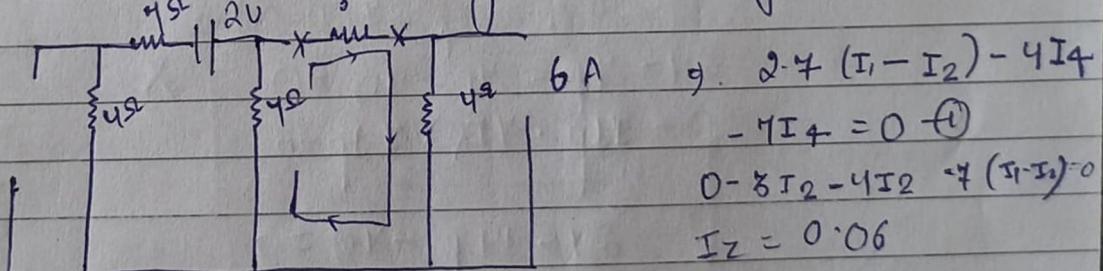Step 4-) Make source 2 for the calculation of current in the desired element by eliminating others sources.




$$9.2 \cdot 4 (I_1 - I_2) - 4I_4 = 0 \quad \text{(1)}$$

$$0 - 8I_2 - 4I_2 + 4(I_1 - I_2) = 0$$

$$I_2 = 0.06 \text{ A}$$

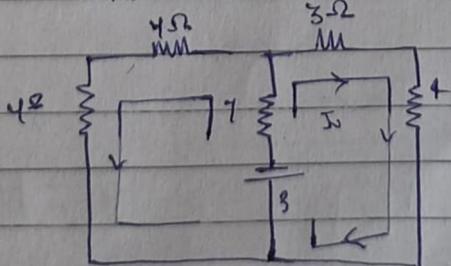$\Rightarrow$  step - 5 Make source 3 ohm & fuse all the sources.



$$3 - 4I_m - 4I_m - 4(I_m + I_N) = 0$$

$$3 - 4I_N - 3I_N - 4(I_N + I_m) = 0$$

$$3 \cdot 4I_m - 7I_m - 7I_m + 7I_N = 0$$

$$3 - 4I_N - 3I_N - 7I_N + 7I_m = 0$$

1.

$$3 - 10I_m + 4I_N = 0$$

$$3 - 4I_N - 4I_m = 0$$

$$\Rightarrow 3 - 10I_m + 4I_N = 0$$

$$3 - 4I_m = 0$$


$$4I_m = 3$$

$$I_m = \frac{1}{4}$$

$$I_m = 0.42$$

$$3 - 10 \times 0.42 + 7 \times 0.42 = 0$$

$$\boxed{I_N = 0.16}$$

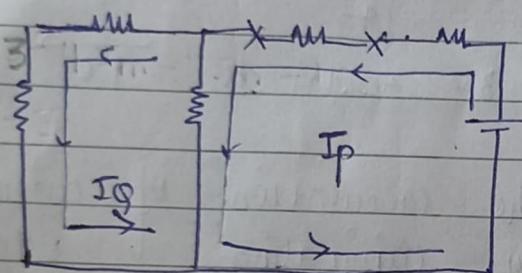

$$24 - 4I_p - 3I_p - 4(I_p - \emptyset) = 0 \quad \textcircled{1}$$

$$0 - 4I_Q - 4I_Q - 4(\emptyset - I_p) = 0$$

$$24 - 4I_p - 3I_p - 4I_p - \emptyset = 0$$

$$24 - 4I_p - 4I_p - \emptyset = 0 \quad X$$

$$0 - 4I_p - 4I_p - \emptyset = 0$$

$$24 - 14I_p - \emptyset = 0$$

$$0 - 18I_p - \emptyset = 0$$

$$\underline{24 - 18 = 32}$$

$$\boxed{24 - 4}$$

$$\begin{array}{r} 14 \\ - 18 \\ \hline 32 \end{array}$$

$$\text{Source } 1 = \overrightarrow{1.10}$$

$$\text{Source } 2 = \overrightarrow{0.06}$$

$$\text{Source } 3 = \overrightarrow{0.16}$$


$$\text{Source } 4 = \overleftarrow{2.10}$$

Find the summation of all current with its direction  
individual sources 1, 2, 3 & 4 in


$$\begin{array}{l} \text{source 1} \quad \overrightarrow{1.10} \\ \text{source 2} \quad \overleftarrow{0.06} \\ \text{source 3} \quad \overleftarrow{0.16} \\ \text{source 4} \quad \overleftarrow{2.10} \end{array} \quad \begin{array}{l} \overrightarrow{1.16} \\ \overleftarrow{2.26} \end{array}$$

Suppose  $\rightarrow 1.10$

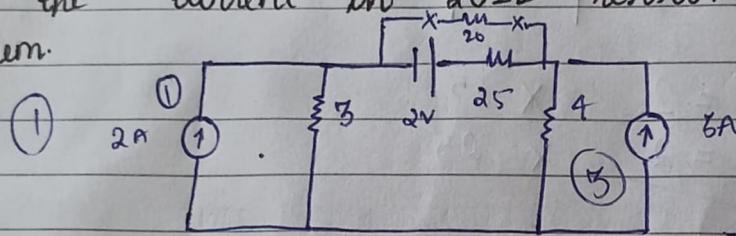Find the current in  $20\Omega$  resistor by superposition theorem.




$$\frac{20 \times 25}{20 + 25} = 1.11$$

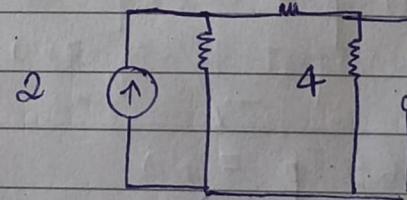

$$I_1 = \frac{2 \times 3}{15.11 + 3} = 0.33$$

$$\frac{6}{18.11} = 0.33$$
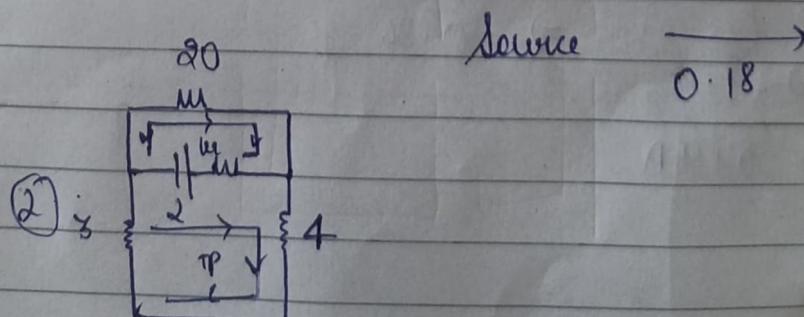
$$\Rightarrow \frac{0.33 \times 25}{20 + 25} = \frac{8.25}{45} = 0.18 \text{ A}$$



$$2 - 25(I_p + I_q) - 4I_p - 3I_p = 0 \quad \text{--- (1)}$$

$$2 - 2s(I_p + I_q) - 20I_q = 0 \quad \text{--- (2)}$$

$$\begin{aligned} 2 - 25I_p + 25I_q - 4I_p - 3I_p \\ 2 - 25I_p + 25I_q - 20I_q = 0 \end{aligned}$$

$$\Rightarrow 2 - 28I_p + 25I_q - 4I_p \\ 2 - 20I_q = 0 \quad | \quad 2 - 25I_p + 5I_q = 0$$


$$\Rightarrow 2 - 32I_p + 25I_q = 0 \\ 2 - 20I_q = 0 \quad | \quad 2 - 25I_p + 5I_q = 0$$

$$\begin{aligned} 32I_p + 25I_q &= 2 & \times 5 \\ 25I_p + 5I_q &= 2 & \times 25 \end{aligned}$$

$$\Rightarrow \begin{aligned} 160I_p + 125I_q &= 10 \\ 625I_p + 125I_q &= 10 \end{aligned} \quad \left. \begin{array}{l} I_p \\ I_q \end{array} \right\} \begin{array}{l} = 0.02 \\ = 0.04 \end{array}$$

$$465I_p = 20$$

$$I_p = 465 / 20$$

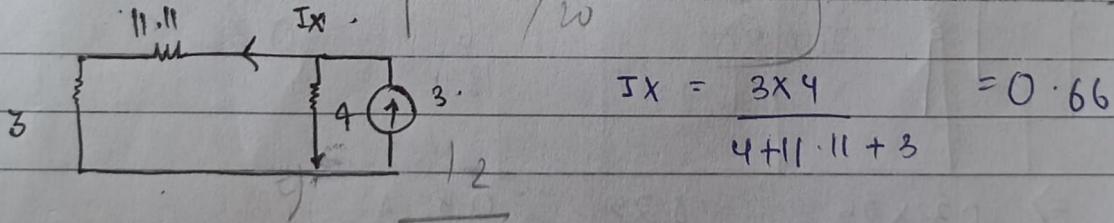

$$I_y = 0.66 \times 25$$

$$[0.66] \Rightarrow 0.36 \quad 25 + 20$$

$$0.37 - 18$$


$$0.19 \text{ A}$$

## Star Delta Transformation :

convert  $\Delta$  to  $\lambda$

$\Delta \rightarrow$  delta

$\lambda \rightarrow$  star

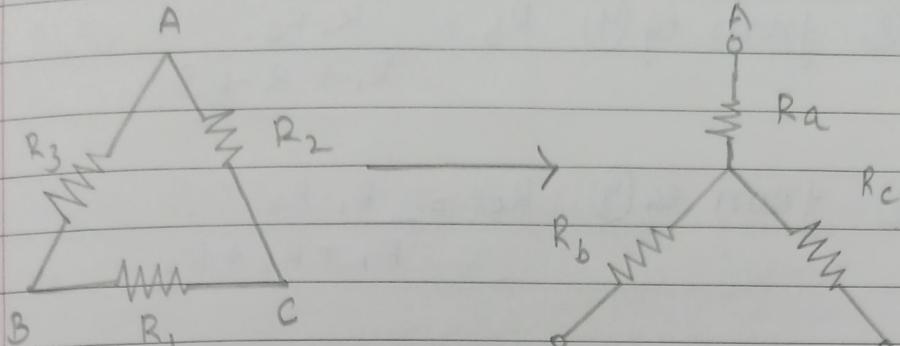

for CA in  $\lambda$

$$R_{CA} = R_A + R_C$$

for CA in  $\Delta$

$$R_{CA} = (R_1 + R_3) \parallel R_2$$

$$R_A + R_C = \frac{(R_1 + R_3) R_2}{R_1 + R_2 + R_3} \quad \textcircled{1}$$

for AB in  $\Delta$

$$R_{AB} = (R_1 + R_2) \parallel R_3$$

$$\frac{(R_1 + R_2) \parallel R_3}{(R_1 + R_2 + R_3)}$$

for AB in  $\lambda$

$$R_{AB} = R_A + R_B$$

$$R_A + R_B = \frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3} \quad \textcircled{2}$$

for BC in  $\lambda$

$$R_{BC} = R_B + R_C$$

for BC in  $\Delta$

$$R_{BC} = (R_2 + R_3) \parallel R_1$$

$$= \left( \frac{(R_2 + R_3) R_1}{R_1 + R_2 + R_3} \right)$$

$$R_B + R_C = \frac{(R_2 + R_3) R_1}{R_1 + R_2 + R_3} \quad \textcircled{3}$$

Adding eq  $\textcircled{1} + \textcircled{2} + \textcircled{3}$

$$R_A + R_B + R_C = \frac{1}{2} \left[ \frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3} + \frac{(R_1 + R_3) R_2}{R_1 + R_2 + R_3} + \frac{(R_2 + R_3) R_1}{R_1 + R_2 + R_3} \right] \quad \textcircled{4}$$


Sub eq ① from eq ④  $R_a = \frac{R_2 + R_3}{R_1 + R_2 + R_3}$

Sub eq ② from eq ④  $R_b = \frac{R_1 R_3}{R_1 + R_2 + R_3}$

Sub eq ③ from eq ④  $R_c = \frac{R_1 R_2}{R_1 + R_2 + R_3}$

Q

Put the value in formula and  
solve A

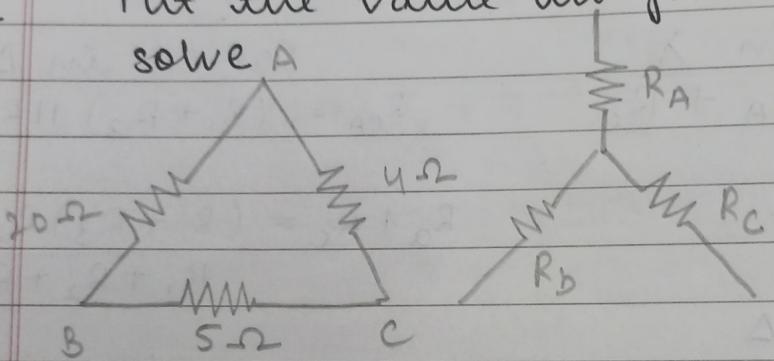

converting  $\lambda$  into  $\Delta$

$$R_a \times R_b = \frac{(R_2 R_3)(R_1 R_3)}{(R_1 + R_2 + R_3)^2} \quad ④$$

$$R_b \times R_c = \frac{(R_1 R_3)(R_1 R_2)}{(R_1 + R_2 + R_3)^2} \quad ⑤$$

$$R_c \times R_a = \frac{(R_2 R_3)(R_1 R_2)}{(R_1 + R_2 + R_3)^2} \quad ⑥$$

Add eq ④, ⑤ and ⑥ will give eq ⑦

$$\Rightarrow \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_b R_c + R_c R_a + R_a R_b}{R_a}$$


$$R_2 = \frac{R_b R_c + R_c R_a + R_a R_b}{R_b}$$

$$R_3 = \frac{R_b R_c + R_c R_a + R_a R_b}{R_c}$$

to calculate eq ⑦

$$\begin{aligned} R_a R_b + R_b R_c + R_c R_a &= \frac{R_1^2 + R_2^2 + R_3^2 + 2(R_1 R_2 + R_2 R_3 + R_1 R_3)}{(R_1 + R_2 + R_3)^2} \\ &= \frac{R_1 R_2 R_3 [R_1 + R_2 + R_3]}{(R_1 + R_2 + R_3)^2} \\ &= \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3} \end{aligned}$$


Step signal | unit step signal  
f(t)

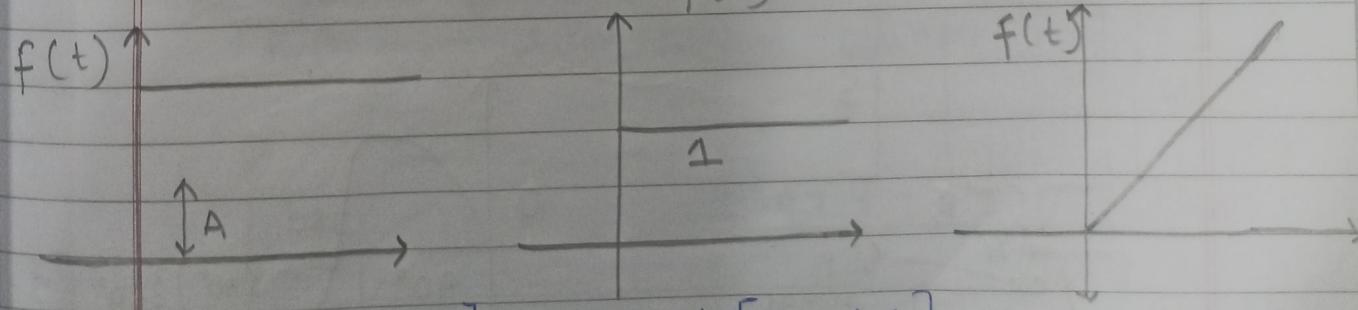


$$f(t) = \begin{cases} A & t > 0 \\ 0 & t \leq 0 \end{cases}$$

$$f(t) \Rightarrow \begin{cases} 1 & t > 0 \\ 0 & t \leq 0 \end{cases}$$


$$f(t) = \begin{cases} At & t > 0 \\ 0 & t \leq 0 \end{cases}$$

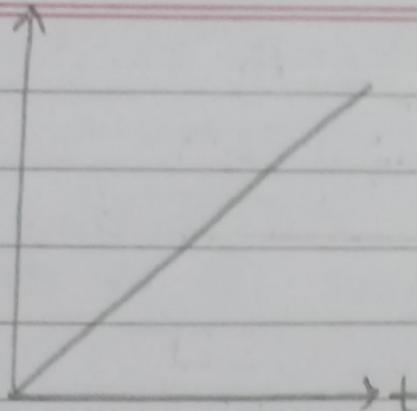$f(t)$ 
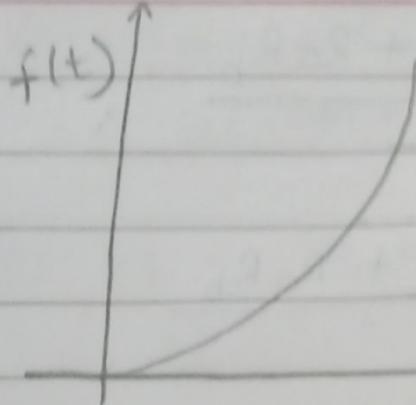
$$f(t) = \begin{cases} t, & t > 0 \\ 0, & t \leq 0 \end{cases}$$



$$f(t) = \begin{cases} At^2, & t > 0 \\ 0, & t \leq 0 \end{cases}$$

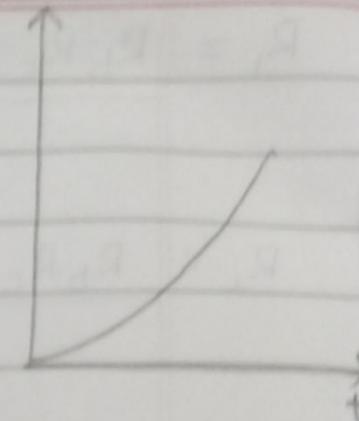 $f(t)$ 

$$f(t) = \begin{cases} t^2, & t > 0 \\ 0, & t \leq 0 \end{cases}$$